

Last Name

First Name

IMPORTANT REMINDERS: You Must show all your work, Must use Mix Logic notations, Write all your assumptions, TTL Manual is not a notebook! All given circuits uses the mix logic notations.

1. Represent 291_{10} in BCD

$$\begin{array}{r} 145 \\ 2 \overline{) 291} \text{ R1} \\ \underline{22} \\ 145 \\ 2 \overline{) 145} \text{ R1} \\ \underline{30} \\ 15 \end{array}$$

$$\begin{array}{r} 18 \\ 2 \overline{) 36} \text{ R0} \\ \underline{9} \\ 18 \\ 2 \overline{) 18} \text{ R0} \\ \underline{4} \\ 9 \\ 2 \overline{) 9} \text{ R1} \\ \underline{2} \\ 4 \\ 2 \overline{) 4} \text{ R0} \\ \underline{2} \\ 2 \\ 2 \overline{) 2} \text{ R0} \end{array}$$

$$2^0 \text{ R1}$$

0010 1001 0001

BCD

6 pt.

$$10010001_2 = 291_{10}$$

$$256 + 32 + 2 + 1 = 291_{10} \checkmark$$

2. Perform the following arithmetic operation in BCD

$$5_{10} + 17_{10} = 22_{10}$$

$$5_{10} = 00101_2$$

$$17_{10} = 10001_2$$

$$\begin{array}{r} 00101_2 \\ + 10001_2 \\ \hline 10110_2 \end{array}$$

$$10110_2 = 22_{10}$$

$$16 + 4 + 2 = 22$$

addition Result

0010 0010

BCD

$$17_{10} + 5_{10} = 22_{10}$$

8 pt.

3. How many 7400 load can the 74LS04 safely drive ?

One. Because 00 is a totem pole TTL so only one output from one 00 can be connected to the input of an 04.

$$n = \frac{I_{OL}}{I_{IL}} = ?$$

$$n = \frac{I_{OH}}{I_{IH}} = ?$$

8 pt.

4. Convert the following equation in to PofS form.

$$F = a'b'c' + a'bc$$

$$F = \overline{a}b\overline{c} + \overline{a}bc$$

a	b	c	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

bc \ a	0	1
00	1	0
01	0	0
10	1	0
11	0	0

$$F = (b + \overline{c})(c + \overline{b})(\overline{a})$$

$$(b + \overline{c})(c + \overline{b})(\overline{a})$$

8 pt.

5. Using circuit in Figure 1;

- Write the equation for F
- Create the K-Map for F
- Convert K-Map in to Truth Table
- Convert the Truth Table into Voltage Table
- Test the circuit for minterms m_0 and m_2 , explain your result

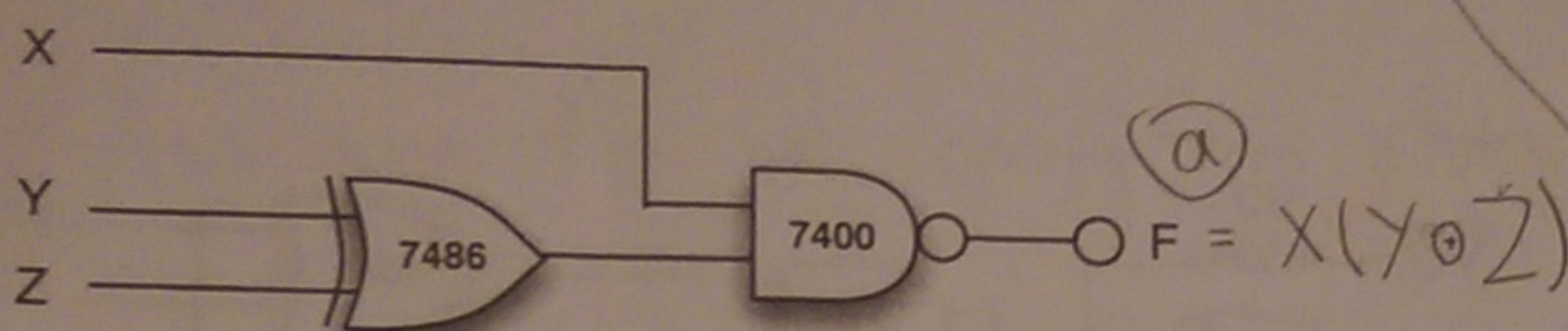


Figure 1

(b) ✓


X \ Z	0	1
0	0	0
1	0	1
2	0	1
3	0	0
4	0	0
5	0	1
6	0	1
7	0	0

(c) ✓

X	Y	Z	F
0	0	0	0
1	0	0	0
2	0	1	0
3	0	1	0
4	1	0	0
5	1	0	1
6	1	1	1
7	1	1	0

(d) ✓

X	Y	Z	F
0	L	L	H
1	L	L	H
2	L	H	H
3	L	H	H
4	H	L	H
5	H	L	L
6	H	H	L
7	H	H	H

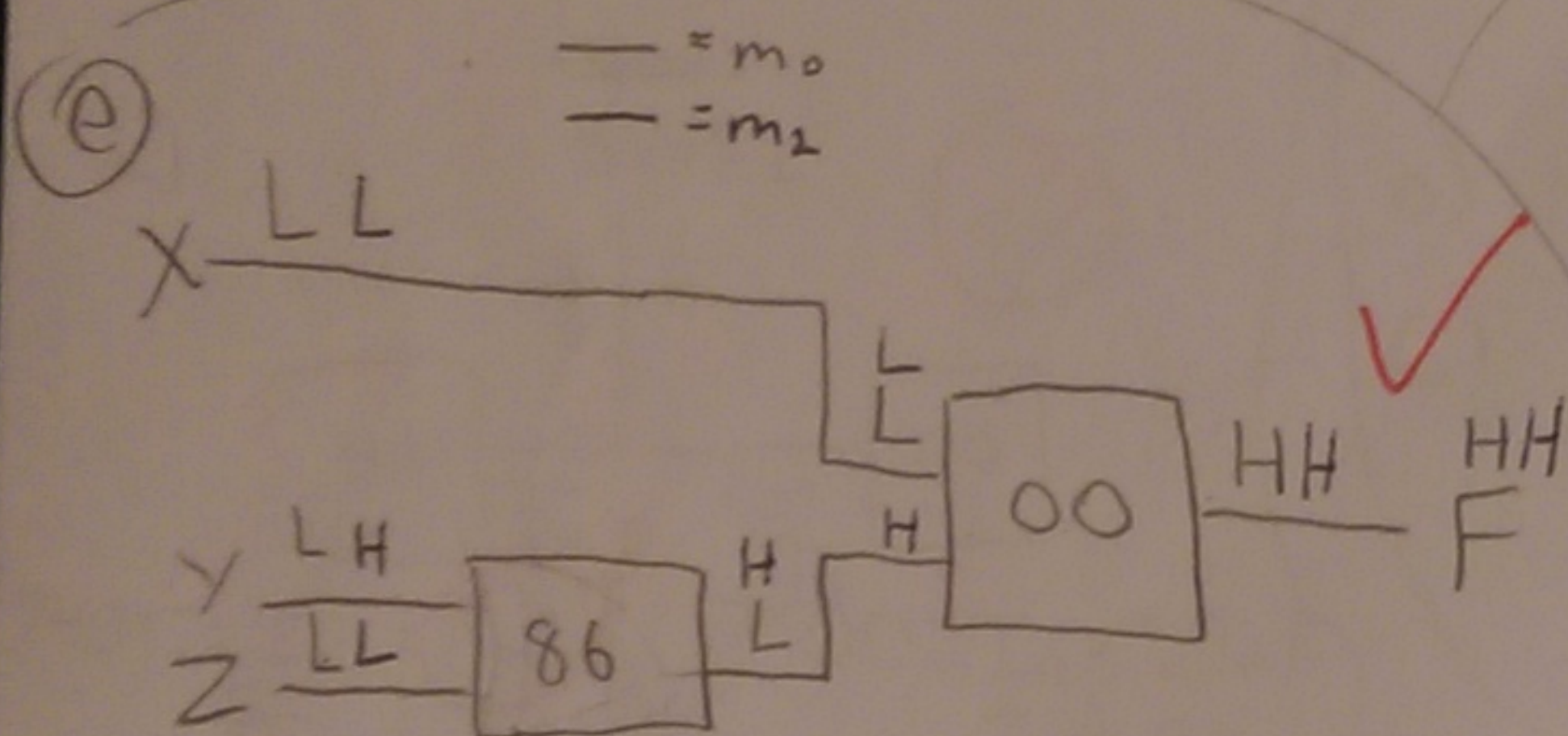

A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

When this circuit was tested with m_0 and m_2 , a resulting voltage high was expected on F.

This result was acquired quickly due to both minterms having a Low on X, as input to a 7400, which always results in a High output voltage.

6. Using circuit in Figure 2;

32pt.

- Verify if the design, if it is not correct make necessary corrections and calculations without changing any of the existing parts.
- Write the equation for F
- Simplify the equation algebraically.

20


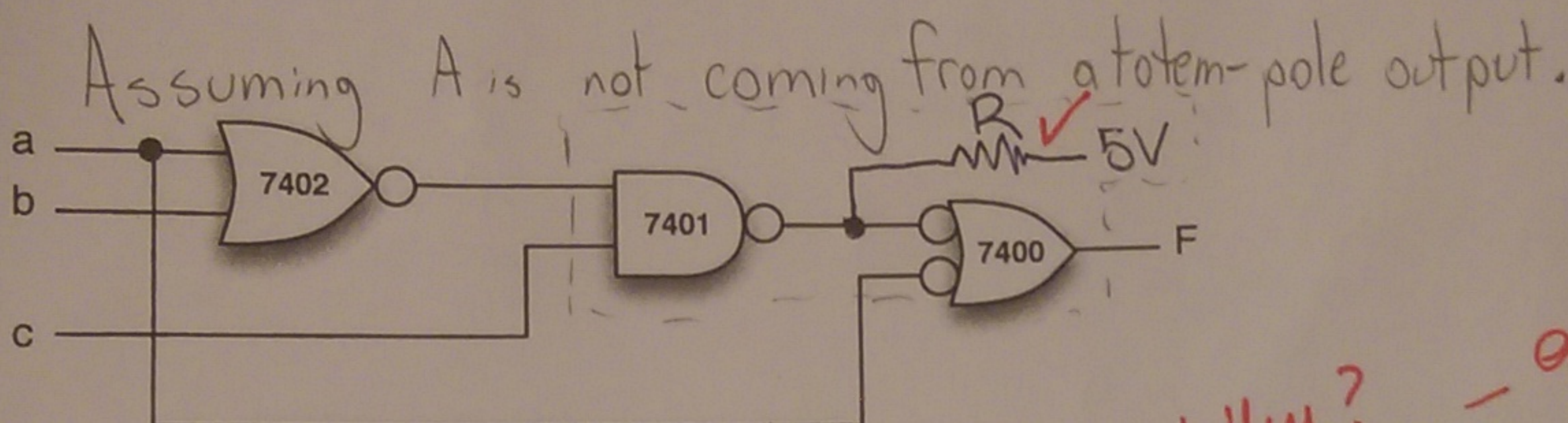


Figure 2

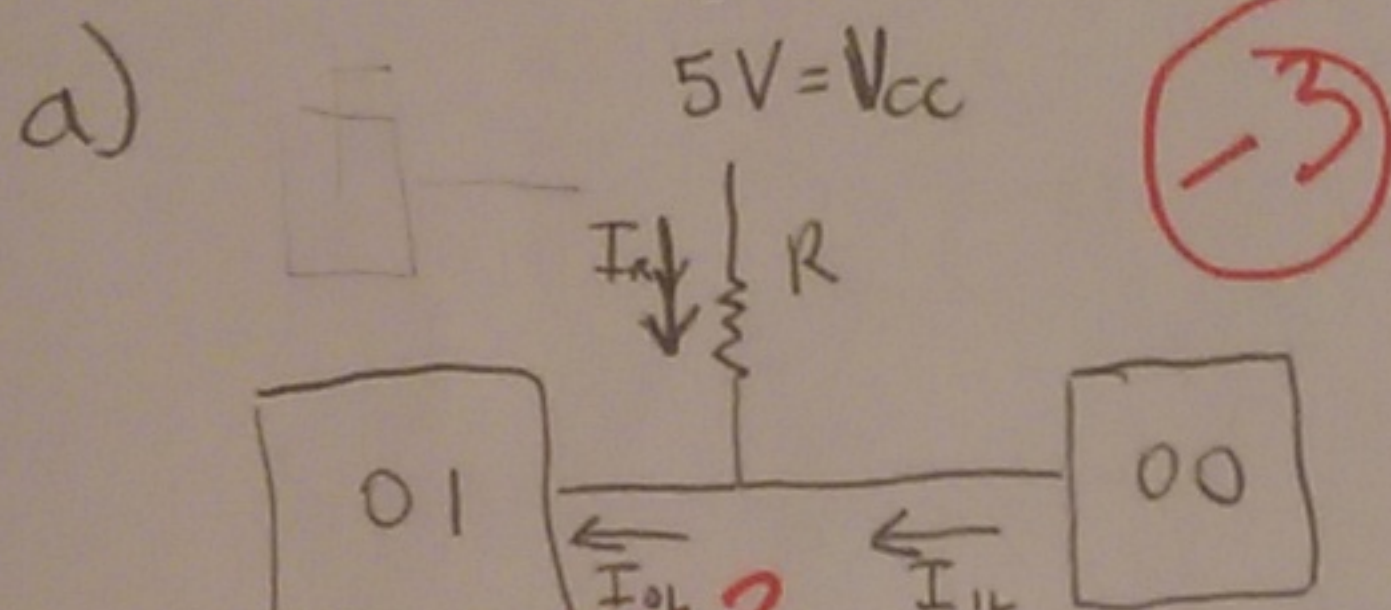

7401: $I_{OL} = 8\text{mA}$ $I_{IL} = 0.4\text{mA}$
 $I_{OH} = 0.1\text{mA}$ $I_{IH} = 20\text{mA}$
 $V_{OL} = 0.5\text{V}$ $V_{OH} = 2.7\text{V}$

Assuming

$$V_{CC} = V_R + V_{OL}$$

$$5\text{V} - 0.5\text{V} = R I_R \rightarrow \frac{4.5\text{V}}{I_R} = \frac{4.5\text{V}}{0.4\text{mA}} = R_{min}$$

$$I_{OL} = I_{IL} + I_R$$

$$0.8\text{mA} - 0.4\text{mA} = I_R$$

$$0.4\text{mA} = I_R$$

$$I_{OH} = I_{IH} + I_R$$

$$0.1\text{mA} - 20\text{mA} = I_R$$

$$80\text{mA} = I_R$$

$$V_{CC} = V_R - V_{OH}$$

$$5\text{V} = V_R - 2.7\text{V}$$

$$5\text{V} - 2.7\text{V} = V_R = I_R R_{max}$$

$$\frac{2.3\text{V}}{I_R} = R_{max} \rightarrow \frac{2.3\text{V}}{80\text{mA}} = R_{max}$$

$$I_R = I_{OH} + I_{IH}$$

b) $F = (\overline{A+B})C + \overline{A}$
 c) $= (\overline{A+B}) + \overline{C} + \overline{A}$
 $= A+B+\overline{C}+\overline{A}$
 $= B+\overline{C}$

$$F = (\overline{a+b}) \cdot c + \overline{a}$$

$$= \overline{a} \overline{b} c + \overline{a}$$

$$= \overline{a} (\overline{b} c + 1)$$

$$F = \overline{a}$$

This circuit will only operate with a pullup resistor added with a value between $\frac{4.5}{400 \times 10^{-6}} \Omega$ and $\frac{2.3}{80 \times 10^{-6}} \Omega$.

Why? # -9