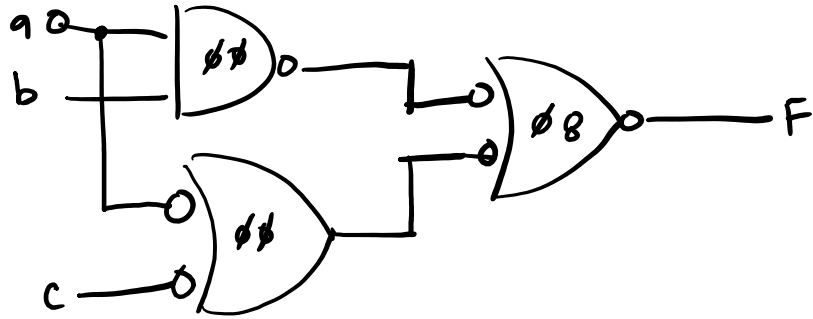


Practice Problems 1

Tuesday, September 13, 2016 3:24 PM

FIND THE EQUATION:




REDESIGN THE CIRCUIT USING ONLY 2'S & 4'S. TEST YOUR CIRCUIT

Practice Problems 1

Thursday, September 15, 2016 4:24 PM

FIND THE EQUATION

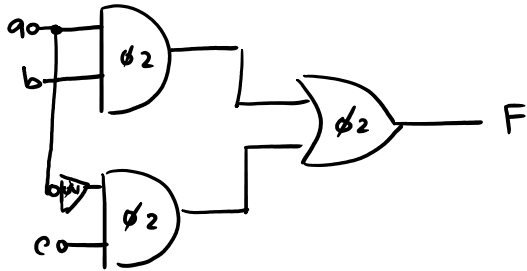

REDO WITH ONLY 2-INPUTS. TEST YOUR CIRCUIT

Practice Problems 1

Thursday, September 15, 2016 4:55 PM

DESIGN A CIRCUIT THAT CAN DETECT BCD (BINARY CODED DECIMAL)