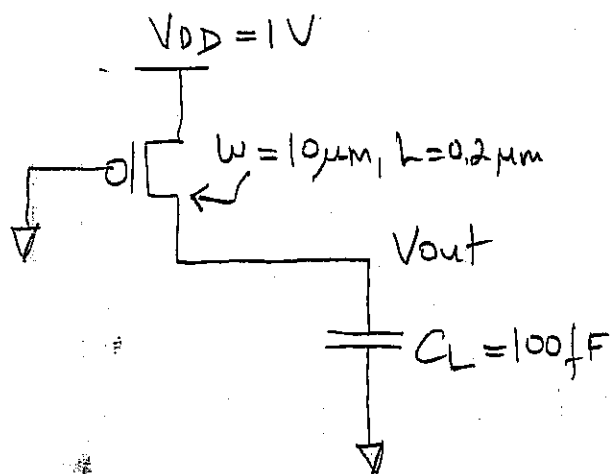


①

40pts



$$\mu_p = 100 \text{ cm}^2/\text{Vsec}$$

$$C_{ox} = 6.9 \times 10^{-7} \text{ F/cm}$$

$$V_{TP} = 0.2V$$

At  $t=0$   $V_{out}=0V \Rightarrow$  plot  $V_{out}(t)$  according to the transistor parameters above. How long does it take for  $V_{out}$  to reach  $1V$ ? Show your calculations clearly.

$$I_D = \frac{\mu_p C_{ox} w}{L} \left[ (V_{SG} - V_{TP}) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$\textcircled{2} \quad Y = A(B + CD)$$

60pts (a) Implement the circuit without using an output inverter.

(b) Assume  $T_R = \frac{T_F}{2} \Rightarrow$  size the transistors according to a minimum geometry of  $1\mu$ .

NOTE = Implement  $Y$  so that you get minimal rise and fall times.

①

$$I_{DSAT} = \frac{\mu_p C_{ox} W}{2L} (V_{SG} - V_{TP})^2$$

$$\mu_p = 100 \text{ cm}^2/\text{Vsec}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-14}}{50 \times 10^{-8}} = 6.9 \times 10^{-7} \text{ F/cm}^2$$

$$V_{SG} = 1 \text{ V} \quad V_{TP} = 0.2 \text{ V}$$


$$W = 10 \mu\text{m} \quad L = 0.2 \mu\text{m}$$

$$I_{DSAT} = \frac{100 \times 6.9 \times 10^{-7} \times 10}{2 \times 0.2} \left( \underbrace{1 - 0.2}_{0.8} \right)^2 = 1.1 \text{ mA}$$

$$C_L = 100 \text{ fF} \Rightarrow T = \frac{100 \times 10^{-15} \times 1}{1.1 \times 10^{-3}} = 90.91 \text{ psec.}$$

②
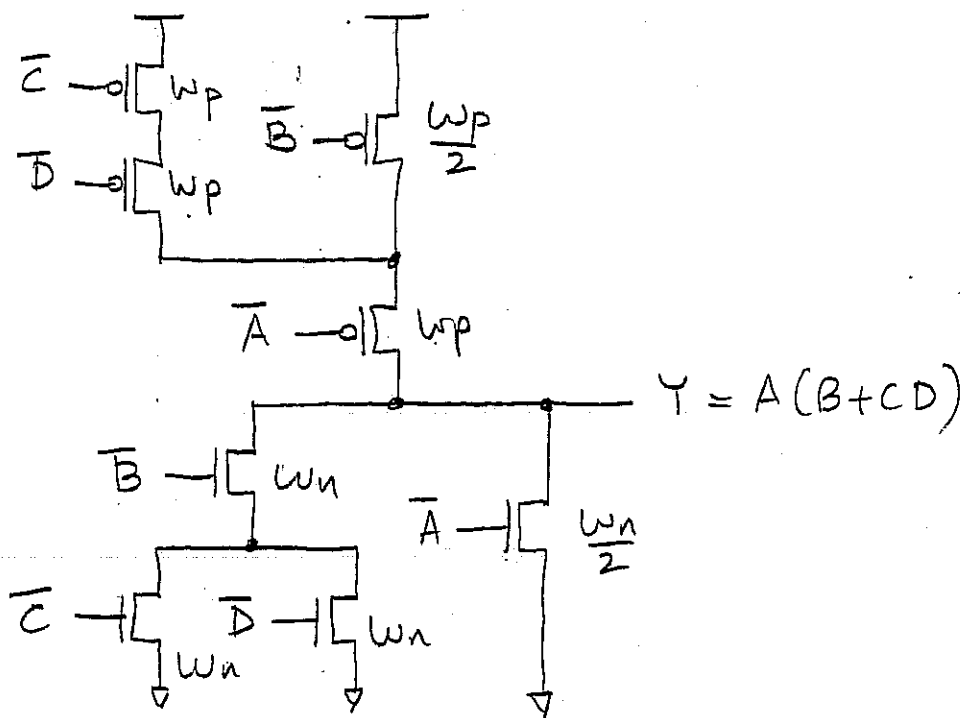
$$(a) \quad Y = A(B + CD) \Rightarrow \overline{Y} = \overline{A} + \overline{(B + CD)} \\ = \overline{A} + \overline{B} \cdot (\overline{C} + \overline{D})$$



$$T_F = 2.2 R_{N_{eq}} C_L = 2.2 C_L 2 R_N = 2.2 C_L \cancel{2} \frac{P}{2\omega_n}$$

$$T_R = 2.2 R_{P_{eq}} C_L = 2.2 C_L 3 R_P = 2.2 C_L 3 \frac{P}{\omega_p}$$


$$T_R = \frac{T_F}{2} \Rightarrow \frac{3}{\omega_p} = \frac{1}{2} \cdot \frac{1}{\omega_n} \Rightarrow \boxed{\omega_p = 6\omega_n}$$

$$\text{Minimum geometry is } 1\mu m \Rightarrow \frac{\omega_n}{2} = 1\mu$$


$$\omega_n = 2\mu$$

$$\omega_p = 12\mu$$

$$\frac{\omega_p}{2} = 6\mu$$

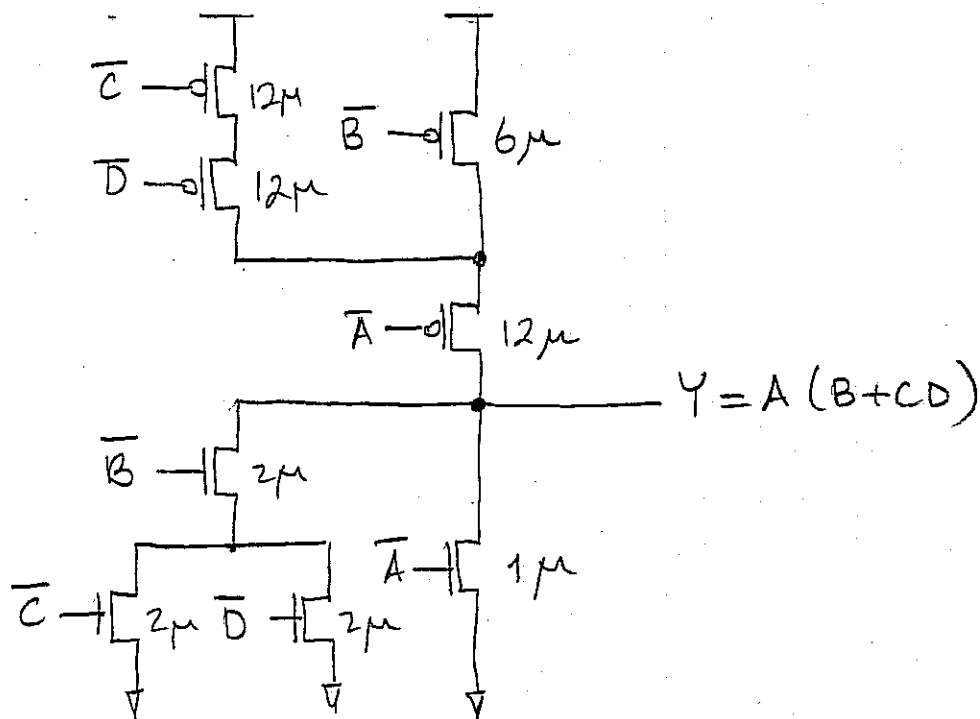


The circuit below is given:

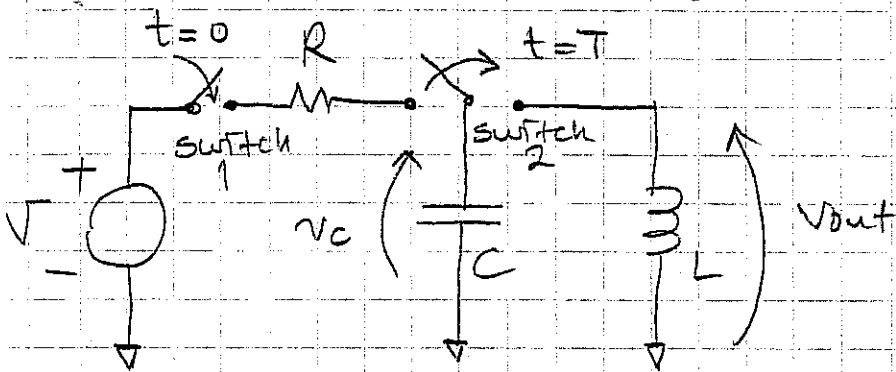


At  $t=0$ , switch 1 is closed; switch 2 is flipped to  $R$  side shown as below.  $v_C(0) = 0 \text{ V}$  &  $i_L(0) = 0 \text{ A}$ .

$t=0$

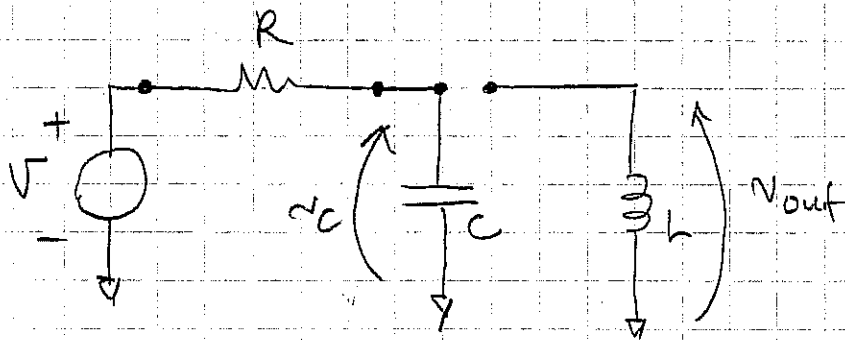


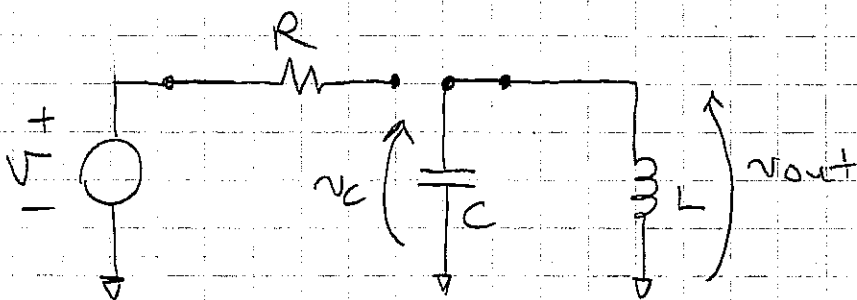At  $t=T$ , while switch 1 is in the same position, switch 2 flips to  $L$  side shown as below:



Find the expression for  $v_{out}(t)$  from  $t=0$  to  $\infty$  & plot it.

Solution:

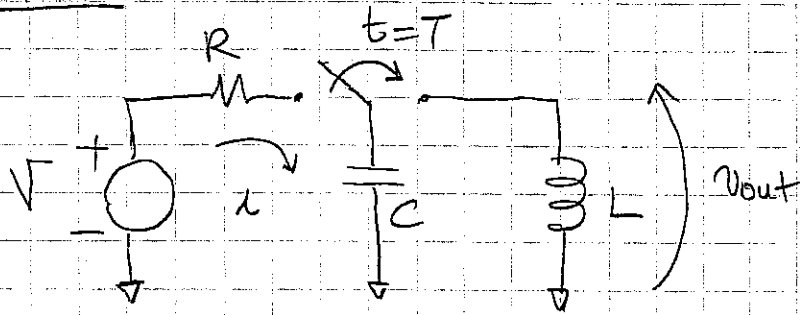

$$V = iR + v_c \rightarrow 0 = R \frac{di}{dt} + \frac{dv_c}{dt} = R \frac{di}{dt} + \frac{1}{C}$$

Thus:

$$\frac{di}{dt} + \frac{i}{RC} = 0 \Rightarrow i = A e^{-\frac{t}{RC}}$$

$$v_c = V - Ri = V - RA e^{-\frac{t}{RC}} \quad \text{but } v_c(0) = 0$$


$$0 = V - RA \Rightarrow A = \frac{V}{R} \Rightarrow i = \frac{V}{R} e^{-\frac{t}{RC}}$$

$$v_c = V(1 - e^{-\frac{t}{RC}})$$

Thus:

$$v_c(T) = V(1 - e^{-\frac{T}{RC}}) \quad \text{as initial condition when the switch is flipped.}$$

$t \geq T$

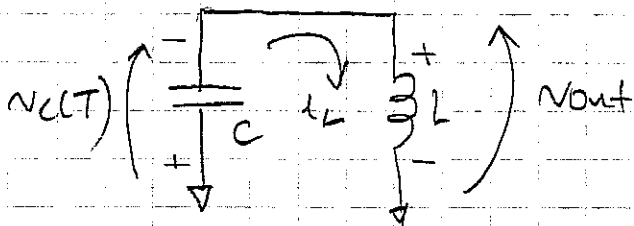

$$v_c + v_L = 0 \Rightarrow \frac{dv_c}{dt} + \frac{dv_L}{dt} = 0 \quad \frac{1}{C} + \frac{d}{dt} \left( L \frac{di_L}{dt} \right) = 0$$

But,


$$V_{out} = L B_1 s_1 e^{s_1(t-T)} - L B_1 s_2 e^{s_2(t-T)}$$

$$= L \left(-\frac{V}{2}\right) j \sqrt{\frac{C}{L}} (1 - e^{-\frac{T}{RC}}) \left[ \frac{j}{\sqrt{LC}} e^{\frac{j}{\sqrt{LC}}(t-T)} + \frac{-j}{\sqrt{LC}} e^{-\frac{j}{\sqrt{LC}}(t-T)} \right]$$

$$= L \left(-\frac{V}{2}\right) j \sqrt{\frac{C}{L}} (1 - e^{-\frac{T}{RC}}) \frac{j}{\sqrt{LC}} \left[ \cos \frac{(t-T)}{\sqrt{LC}} + \cancel{j \sin \frac{(t-T)}{\sqrt{LC}}} \right. \\ \left. + \cos \frac{(t-T)}{\sqrt{LC}} - \cancel{j \sin \frac{(t-T)}{\sqrt{LC}}} \right]$$

$$= \cancel{L} \cancel{\left(-\frac{V}{2}\right)} \cancel{j} \cancel{\sqrt{\frac{C}{L}}} (1 - e^{-\frac{T}{RC}}) \frac{1}{\cancel{\sqrt{LC}}} \cdot \cancel{2} \cos \frac{(t-T)}{\sqrt{LC}}$$
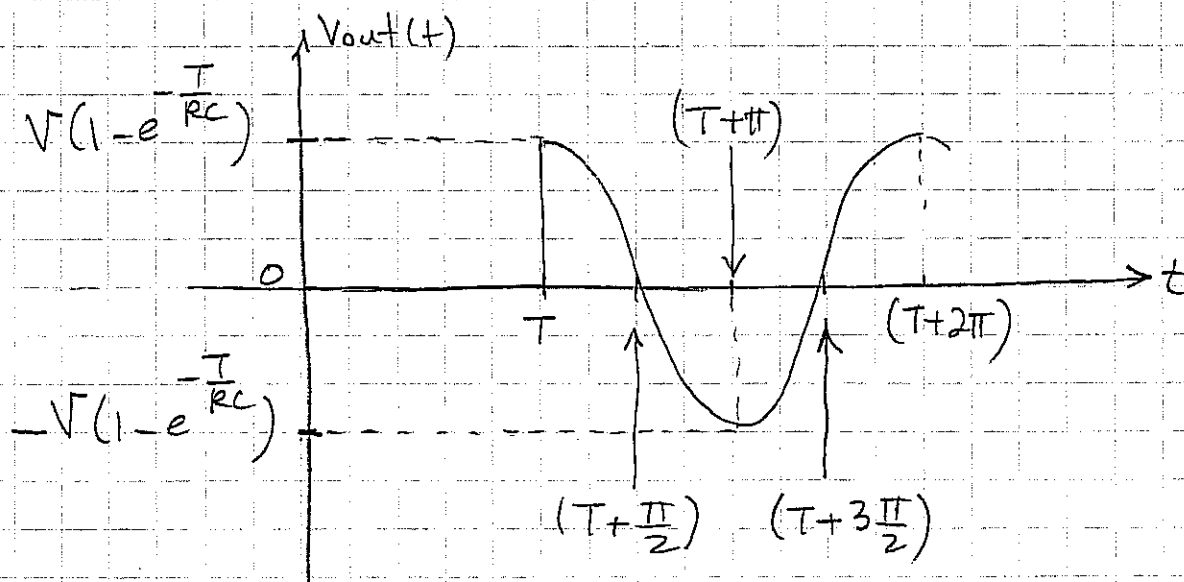
$$V_{out} = V (1 - e^{-\frac{T}{RC}}) \cos \frac{(t-T)}{\sqrt{LC}}$$



$$\frac{d^2 i_L}{dt^2} + \frac{i_L}{LC} = 0 \quad s^2 + \frac{1}{LC} = 0 \quad s_1 = \frac{j}{\sqrt{LC}}, \quad s_2 = -\frac{j}{\sqrt{LC}}$$

$$i_L = B_1 e^{s_1(t-T)} + B_2 e^{s_2(t-T)}$$

$$v_{out} = L \frac{di_L}{dt} = L B_1 s_1 e^{s_1(t-T)} + L B_2 s_2 e^{s_2(t-T)}$$

$$v_{out}(T) = v_C(T) = V(1 - e^{-\frac{T}{RC}}) \Rightarrow$$

$$\frac{V}{L}(1 - e^{-\frac{T}{RC}}) = B_1 s_1 + B_2 s_2 \quad \text{--- Eqn. 1}$$

We also know that  $i_L(T) = 0 \text{ A}$

$$0 = B_1 + B_2 \quad \text{--- Eqn. 2}$$

Substitute  $B_2 = -B_1$  in Eqn. 1



$$\frac{V}{L}(1 - e^{-\frac{T}{RC}}) = B_1(s_1 - s_2) \Rightarrow B_1 = \frac{V}{L} \frac{(1 - e^{-\frac{T}{RC}})}{(s_1 - s_2)}$$

$$\text{But, } s_1 - s_2 = \frac{j}{\sqrt{LC}} + \frac{j}{\sqrt{LC}} = \frac{2j}{\sqrt{LC}} \Rightarrow$$

$$B_1 = \frac{V}{L} \frac{(1 - e^{-\frac{T}{RC}})}{2j} \cdot \sqrt{LC} = -\frac{V}{2} j \sqrt{\frac{C}{L}} (1 - e^{-\frac{T}{RC}})$$

$$B_2 = \frac{V}{2} j \sqrt{\frac{C}{L}} (1 - e^{-\frac{T}{RC}})$$



①

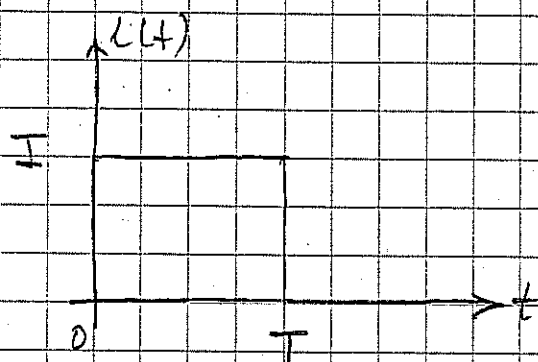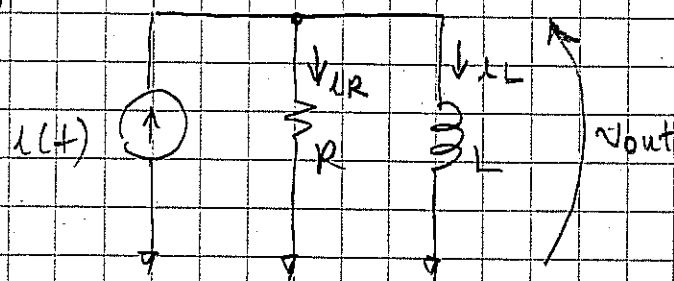

30pts (a) Solve  $i_L(t)$  and  $v_{out}(t)$  using time-domain analysis

20pts (b) Plot  $i_L(t)$  and  $v_{out}(t)$

②

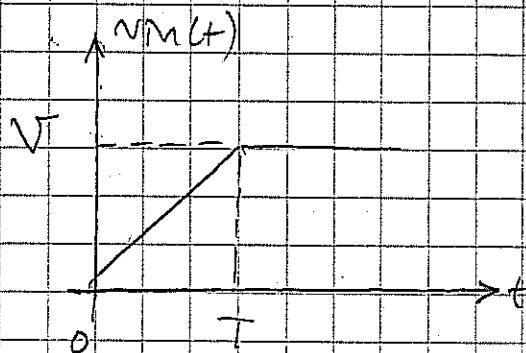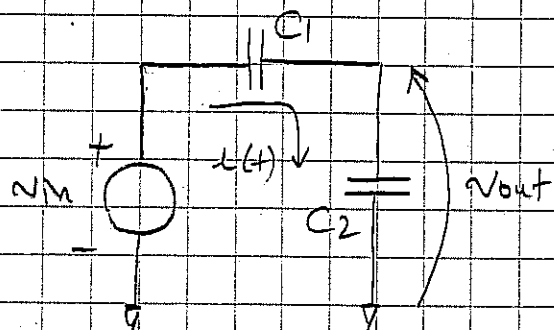


30pts (a) Solve  $i(t)$  and  $v_{out}(t)$  using time-domain analysis

20pts (b) Plot  $i(t)$  and  $v_{out}(t)$



①  
(a)

For  $t \leq T$ :

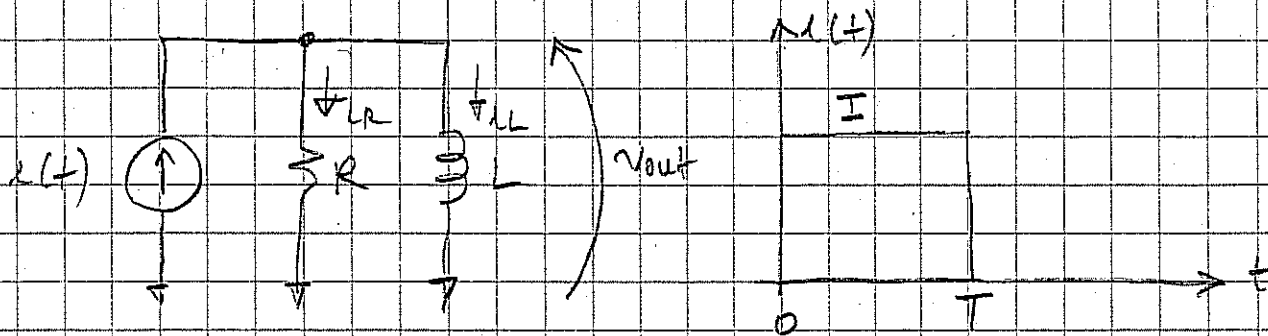

$$\left. \begin{aligned} i(t) &= i_R + i_L \\ i_R &= \frac{v_{out}}{R} \\ v_{out} &= L \frac{di_L}{dt} \end{aligned} \right\} \quad \begin{aligned} L \frac{di_L}{dt} + R i_L &= L \frac{di_L}{dt} \\ i_R &= \frac{L}{R} \frac{di_L}{dt} \end{aligned}$$

$$i(t) = \frac{L}{R} \frac{di_L}{dt} + i_L \quad \text{or} \quad \frac{di_L}{dt} + \frac{R}{L} i_L = \frac{R}{L} i(t)$$

$$i_L(t) = A e^{-\frac{R}{L}t} + i_{part} \quad \text{where } i_{part} = I$$

$$i_L(t) = A e^{-\frac{R}{L}t} + I, \quad \text{but } i_L(0) = 0 = A + I$$

$$i_L(t) = I \left(1 - e^{-\frac{R}{L}t}\right) \Rightarrow v_{out} = I L \left[0 - e^{-\frac{R}{L}t} \cdot \left(-\frac{R}{L}\right)\right] = I R e^{-\frac{R}{L}t}$$

For  $t \geq T$ :  $\frac{di_L}{dt} + \frac{R}{L} i_L = 0$  since  $i(t \geq T) = 0$  A



$$i_L = B e^{-\frac{R}{L}(t-T)} \quad \text{But, } i_L(T) = I \left(1 - e^{-\frac{R}{L}T}\right) = B \text{ for } t \leq T$$

$$i_L(t) = I \left(1 - e^{-\frac{R}{L}T}\right) e^{-\frac{R}{L}(t-T)}$$

$$v_{out} = I \left(1 - e^{-\frac{R}{L}T}\right) e^{-\frac{R}{L}(t-T)} \left(-\frac{R}{L}\right) = -I R \left(1 - e^{-\frac{R}{L}T}\right) e^{-\frac{R}{L}(t-T)}$$


Continue ①

(b)  $i_L(t)$

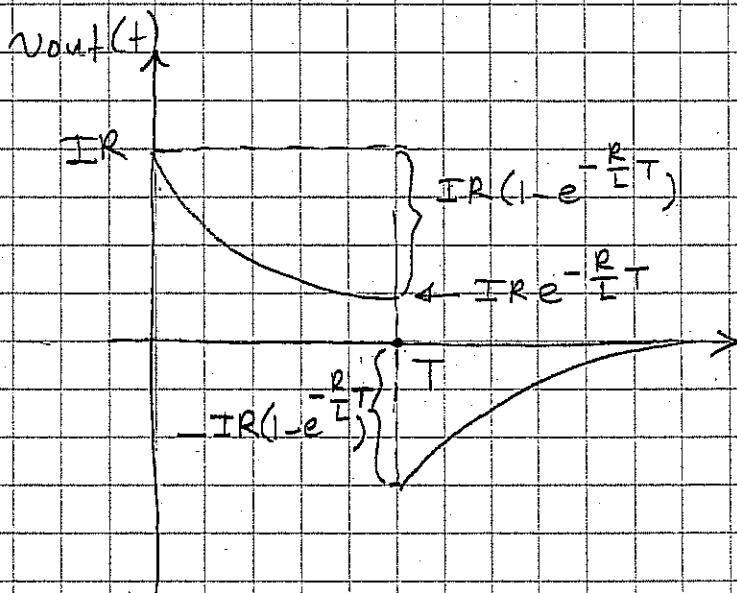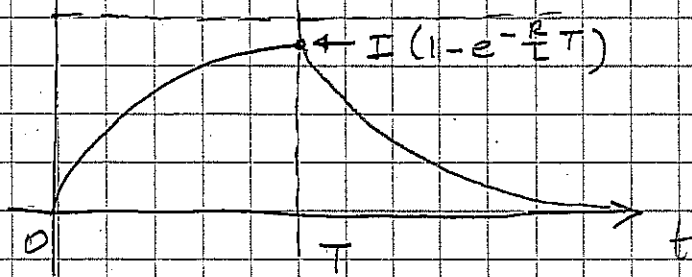

(2)

(a)

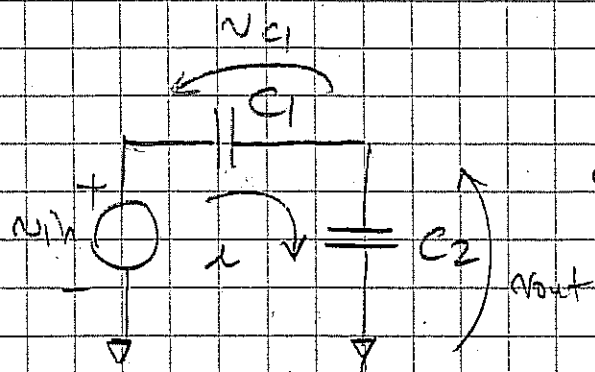

$$v_M = v_{C1} + v_{out} \Rightarrow \frac{dv_M}{dt} = \frac{dv_{C1}}{dt} + \frac{dv_{out}}{dt}$$

$$\text{Thus; } \frac{dv_M}{dt} = \frac{i}{C1} + \frac{i}{C2}$$

$$i = \frac{C1 C2}{(C1 + C2)} \frac{dv_M}{dt}$$

From the graph -

$$v_M(t) = \frac{V}{T} t \quad 0 \leq t \leq T$$

$$= V \quad t \geq T$$

$$\text{Thus: } \frac{dv_M}{dt} = \frac{V}{T} \Rightarrow i = \frac{C1 C2}{(C1 + C2)} \frac{V}{T} \text{ for } 0 \leq t \leq T$$

$$\text{Since } i = C2 \frac{dv_{out}}{dt} \Rightarrow v_{out} = \frac{1}{C2} \int_0^t i(t) dt$$




$$= \frac{1}{C2} \cdot \frac{C1 C2}{(C1 + C2)} \frac{V}{T} t$$

$$\Rightarrow v_{out} = \frac{C1}{(C1 + C2)} V \text{ for } 0 \leq t \leq T$$


$$\text{For } t \geq T \quad v_M(t) = V \quad \frac{dv_M}{dt} = 0 \Rightarrow i = 0 \text{ A}$$

$$v_{out} = \frac{C1}{C1 + C2} V$$

(b)

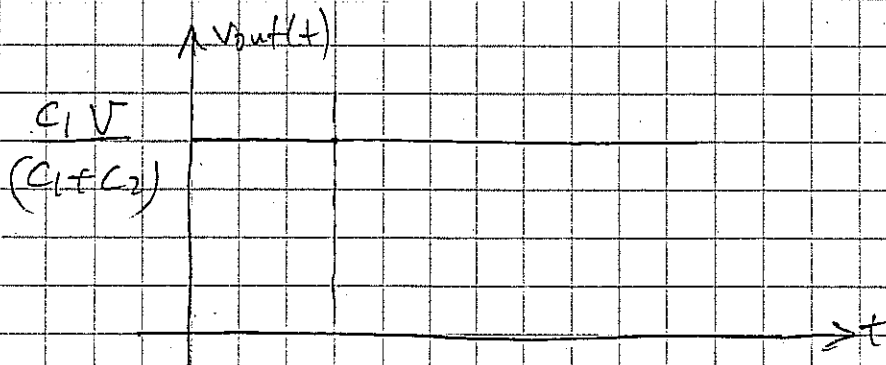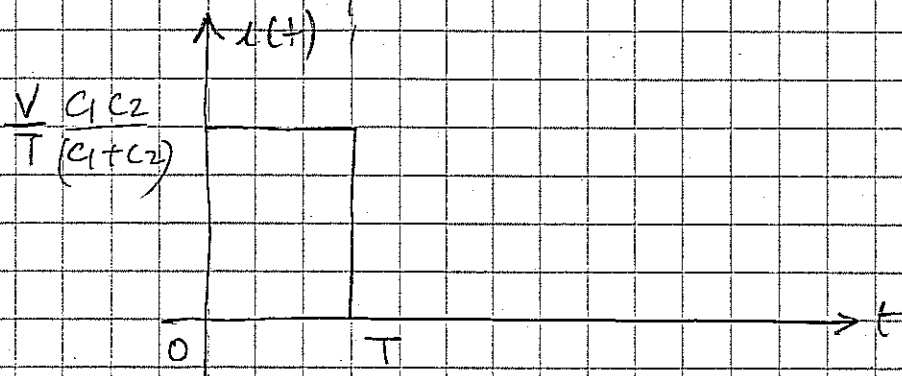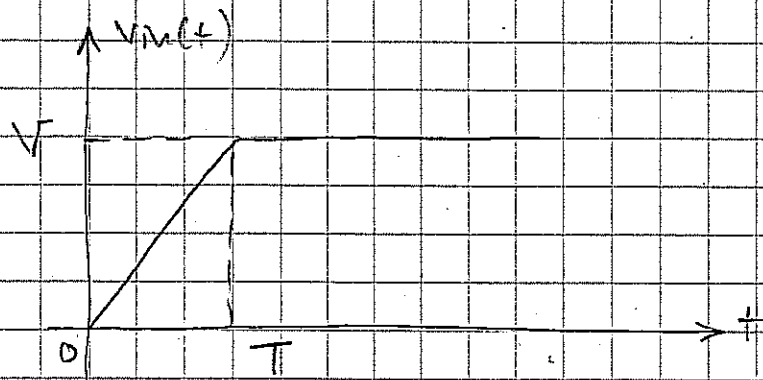

① Consider the circuit below:

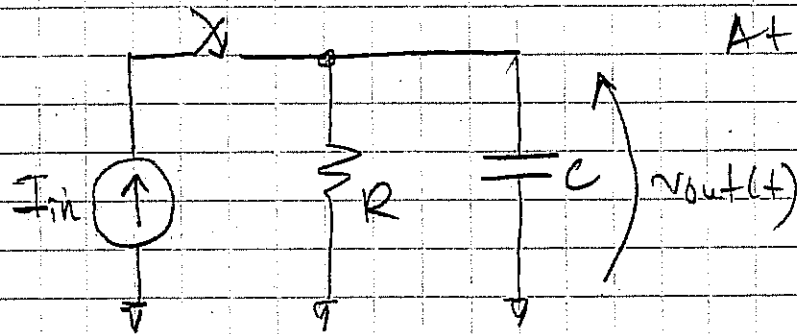


At  $t=0^+$  switch closes.

$$v_{out}(0) = 0 \text{ V}$$

$I_M$  is a constant current

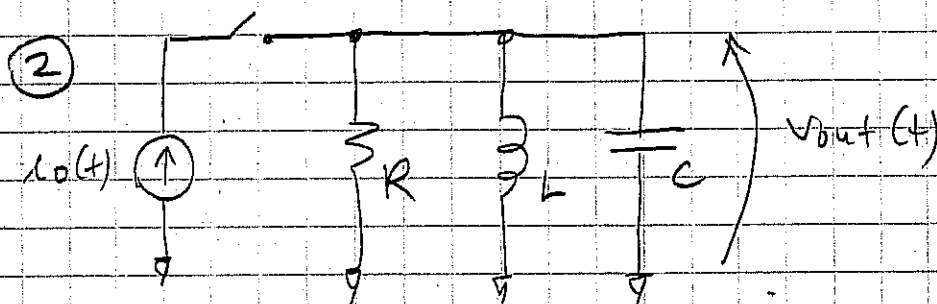Using time-domain analysis, derive  $v_{out}(t)$  & plot it.



(a) Find  $H(s) = \frac{V_{out}(s)}{I_o(s)}$  & find the poles


(b) Find the value of  $R$  in terms of  $L$  &  $C$  such that  
 the circuit is stable but  $v_{out}$  undershoots (overdamped)  
 the circuit is stable but  $v_{out}$  is critical (critically damped)  
 & the circuit is stable but  $v_{out}$  overshoots (underdamped).

Plot the location of poles & approximate  $v_{out}$  for each case

(c) What is the value of  $R$  to make the circuit oscillatory?

Find the frequency of oscillation. Plot the location of pole


①

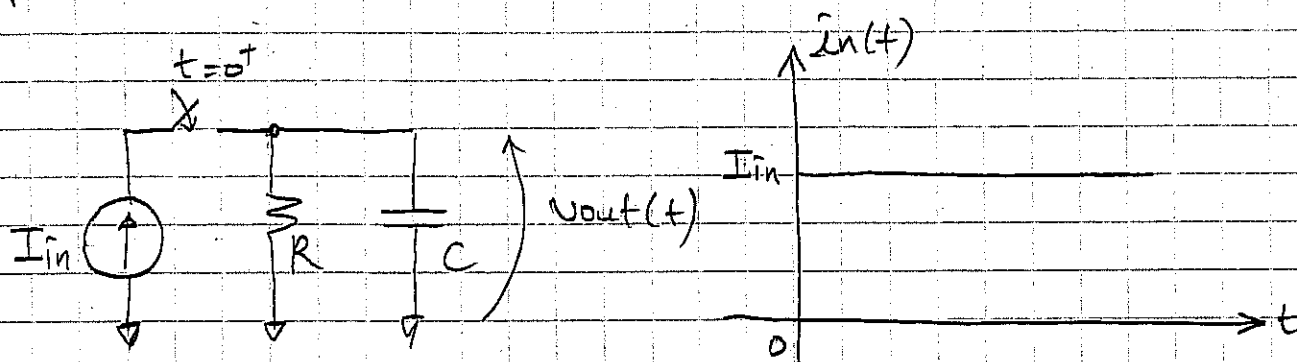

$$v_{out}(0) = 0 \text{ V}$$

$$\left. \begin{aligned} I_{in} &= I_R + I_C \\ v_{out} &= I_R R \\ I_C &= C \frac{dv_{out}}{dt} \end{aligned} \right\} \quad I_{in} = \frac{v_{out}}{R} + C \frac{dv_{out}}{dt}$$
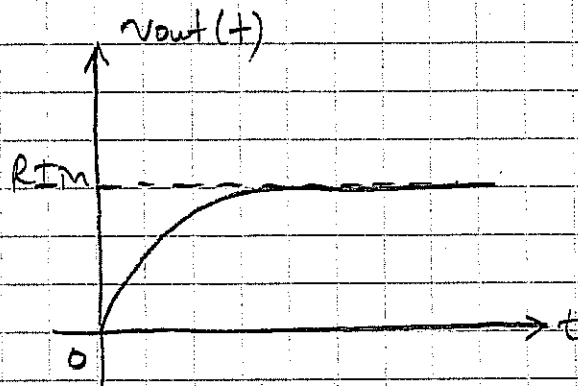
$$\frac{dv_{out}}{dt} + \frac{1}{RC} v_{out}(t) = \frac{I_{in}}{C}$$



$$v_{out} = v_{out_{gen}} + v_{out_{part}}$$

$$v_{out_{gen}} = A e^{st} \quad v_{out_{part}} = K$$

$$\text{Char. eqn: } s + \frac{1}{RC} = 0 \Rightarrow s = -\frac{1}{RC}$$


$$v_{out_{gen}} = A e^{-\frac{t}{RC}}$$

$$\text{For } v_{out_{part}} = \frac{1}{R} \cdot K = \frac{I_{in}}{C} \Rightarrow K = R I_{in}$$

$$v_{out} = A e^{-\frac{t}{RC}} + R I_{in}$$

$$v_{out}(0) = A + R I_{in} = 0 \Rightarrow A = -R I_{in}$$
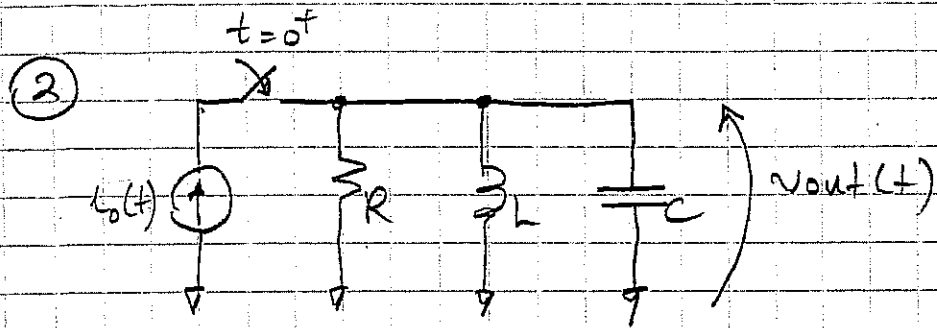
$$v_{out}(t) = R I_{in} (1 - e^{-\frac{t}{RC}})$$



$$(a) \quad I_0(s) = I_R(s) + I_L(s) + I_C(s)$$

$$= \frac{V_{out}(s)}{R} + \frac{V_{out}(s)}{sL} + V_{out}(s) \cdot sC = V_{out}(s) \left( \frac{1}{R} + \frac{1}{sL} + sC \right)$$

$$I_0(s) = V_{out}(s) \cdot \frac{s^2 LCR + R + sL}{sRL} = V_{out}(s) \cdot \frac{LCR(s^2 + s/RC + 1/LC)}{sRL}$$

$$H(s) = \frac{V_{out}(s)}{I_0(s)} = \frac{s}{C(s^2 + \frac{s}{RC} + \frac{1}{LC})}$$

$$\text{Poles: } s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad s_{1,2} = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$$


$$= -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\text{Let } \alpha \triangleq \frac{1}{2RC}, \omega_0 \triangleq \frac{1}{\sqrt{LC}} \Rightarrow$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$(b) \quad (1) \quad \text{If } \alpha > \omega_0 \Rightarrow \frac{1}{2RC} > \frac{1}{\sqrt{LC}} \Rightarrow R < \frac{\sqrt{LC}}{2C} \Rightarrow R < \frac{1}{2} \sqrt{\frac{L}{C}}$$

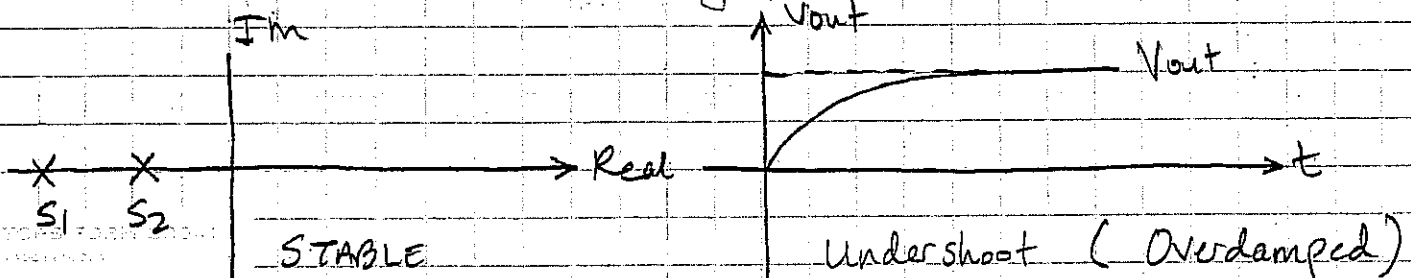Then, both roots lay on the LHS real axis




$$(2) \alpha = \omega_0 \quad s_{1,2} = -\alpha \Rightarrow R = \frac{1}{2} \sqrt{\frac{L}{C}}$$

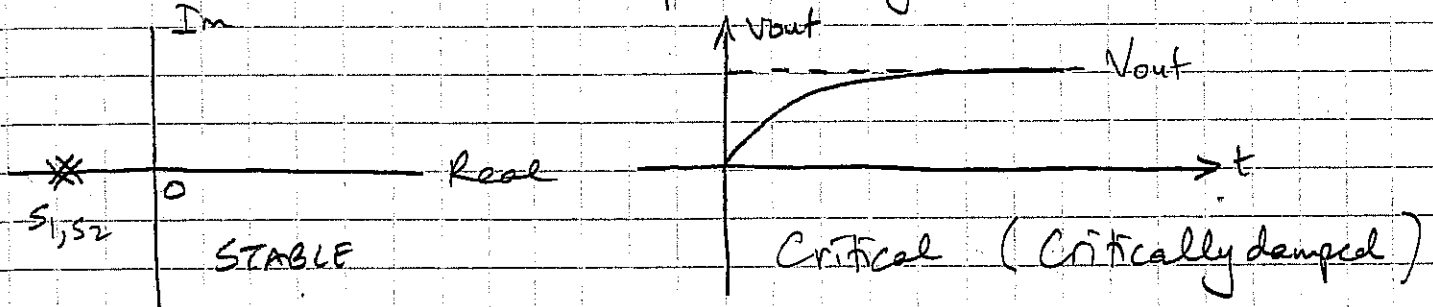Then both roots are equal & lay on the LHS real axis.




$$(3) \alpha < \omega_0 \quad s_{1,2} = -\alpha \pm j \sqrt{\omega_0^2 - \alpha^2} \Rightarrow R > \frac{1}{2} \sqrt{\frac{L}{C}}$$

Then the roots lay on the LHS plane

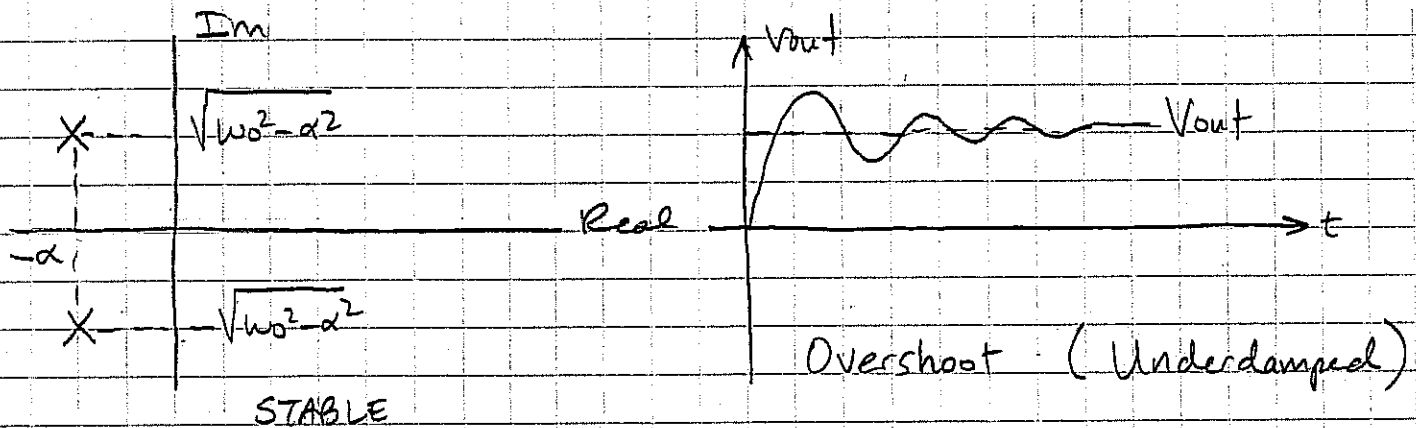

$$(c) \text{ If } R = \infty \Omega \text{ (open circuit)} \Rightarrow \alpha = 0$$

$$s_{1,2} = \pm j \omega_0$$

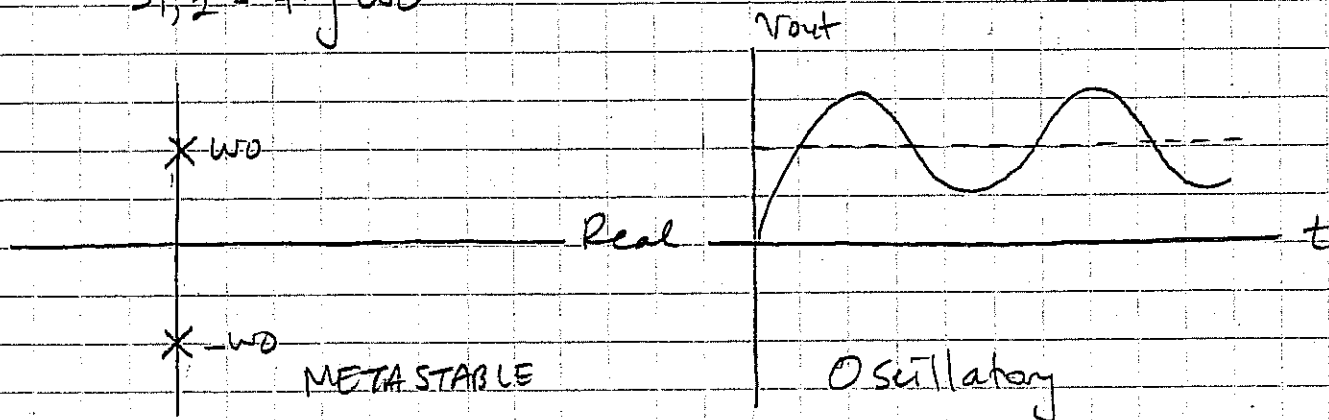

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \text{oscillation frequency.}$$



Design the following logic function and size the transistors such that  $T_R = 2 T_F$ .

$$f = \overline{A}B + C$$

NOTE: Do NOT consider Elmore delay components.  
Do NOT use any inverters at the output.


Solution:

Since we are not allowed to use any inverters at the output we need to find out  $\overline{f}$ .

$$f = \overline{A} \cdot B + C$$

$$\overline{f} = \overline{\overline{A} \cdot B + C}$$
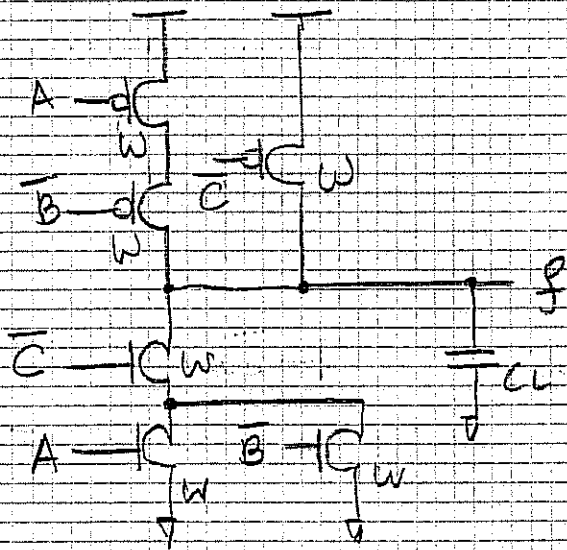
$$= (A + \overline{B}) \cdot \overline{C}$$



$$T_F = 2.2 C_L R_{\text{eq}} = 2.2 C_L (R_n + R_p) \\ = 2.2 C_L (2 R_n)$$



$$T_R = 2.2 C_L R_{\text{eq}} = 2.2 C_L (R_p + R_p) \\ = 2.2 C_L (2 R_p)$$

$$2 T_F = T_R \Rightarrow 2 R_n = R_p$$

$$R_n = \frac{K}{2 W_n} \quad R_p = \frac{K}{W_p}$$


$$2 \frac{K}{2 W_n} = \frac{K}{W_p} \Rightarrow \boxed{W_p = W_n = W}$$

1.

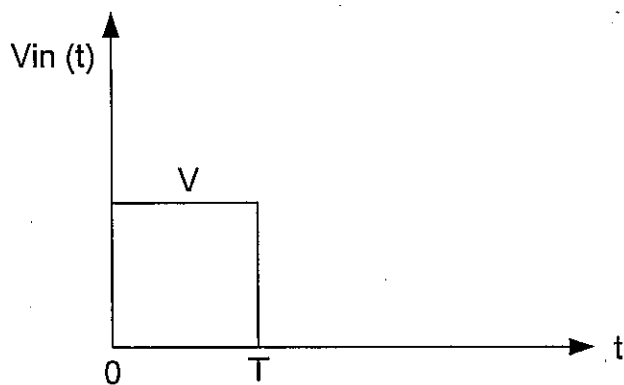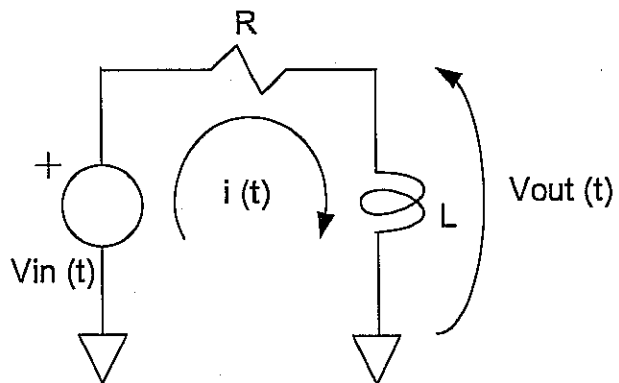


- (a) If  $V_{in}(t)$  is given above, find  $i(t)$  using time-domain analysis. Note that  $i(0) = 0$  in the inductor.
- (b) Compute  $V_{out}(t)$  using time-domain analysis.

2.

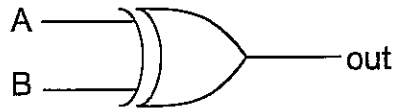

- (a) Write output function of this gate in terms of its inputs, A and B (Form a min-term function).
- (b) Implement the above gate with CMOS circuitry.

# EMPE110 MIDTERM solutions:

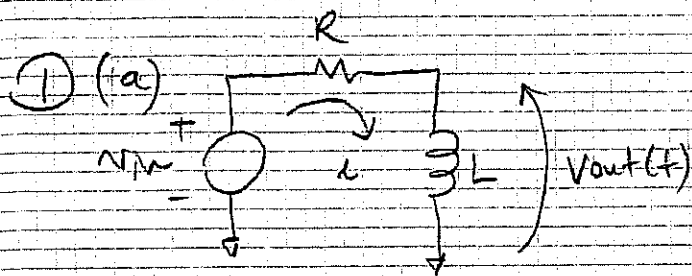

$0 \leq t \leq T$ :

$$V = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L}i = \frac{V}{L}$$

general soln:  $\frac{di_g}{dt} + \frac{R}{L}i_g = 0$

$$s + \frac{R}{L} = 0 \quad s = -\frac{R}{L}$$

$$i_g(t) = A e^{-\frac{R}{L}t}$$


particular soln:

$$i_p(t) = K$$

$$0 + \frac{R}{L}K = \frac{V}{L} \Rightarrow K = \frac{V}{R}$$

Thus:  $i = i_g + i_p = A e^{-\frac{R}{L}t} + \frac{V}{R}$


At  $t=0$  the circuit looks like:

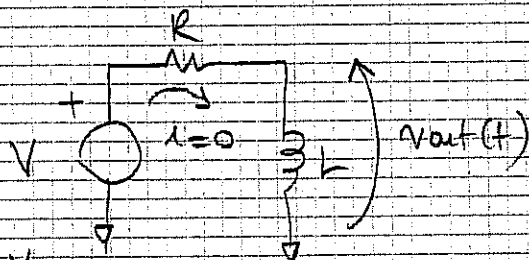

$$i(0) = A + \frac{V}{R} = 0 \Rightarrow A = -\frac{V}{R}$$

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}t}) \quad 0 \leq t \leq T$$

$T \leq t < \infty$ :

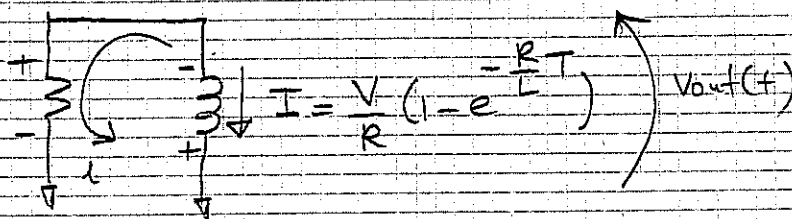

$$VR + VL = 0 \Rightarrow iR + L \frac{di}{dt} = 0$$

$$i(t) = B e^{-\frac{R}{L}(t-T)} \quad \text{but} \quad i(T) = I = B$$

Thus:



$$i(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}T}) e^{-\frac{R}{L}(t-T)}$$

$$(b) \quad v_{out} = L \frac{di}{dt} = L \frac{V}{R} \left[ 0 - e^{-\frac{R}{L}t} \cdot \left(-\frac{R}{L}\right) \right] = \cancel{L} \frac{V}{\cancel{R}} \cdot \frac{\cancel{R}}{\cancel{L}} e^{-\frac{R}{L}t}$$

$$v_{out} = V e^{-\frac{R}{L}t} \quad 0 \leq t \leq T$$


However for  $T \leq t < \infty$ :
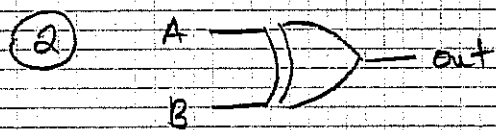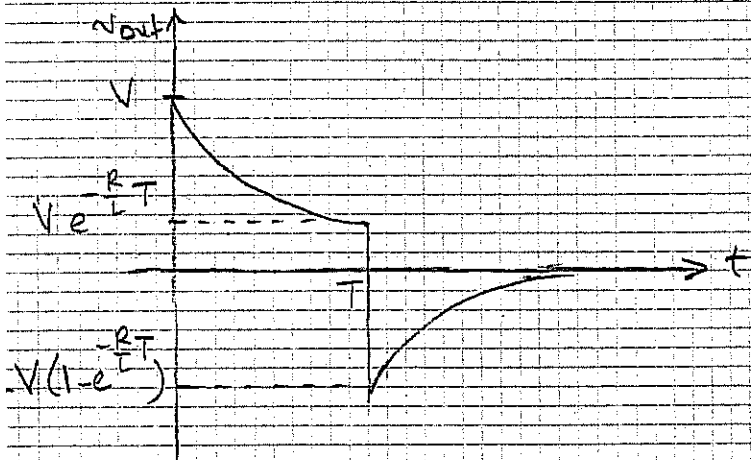
$$\begin{aligned} v_{out} &= L \frac{di}{dt} = \frac{V}{R} (1 - e^{-\frac{R}{L}T}) \left(-\frac{R}{L}\right) e^{-\frac{R}{L}(t-T)} \cdot \cancel{L} \\ &= -V (1 - e^{-\frac{R}{L}T}) e^{-\frac{R}{L}(t-T)} \end{aligned}$$




(a)  $out = A \oplus B = A\bar{B} + \bar{A}B$

(b)

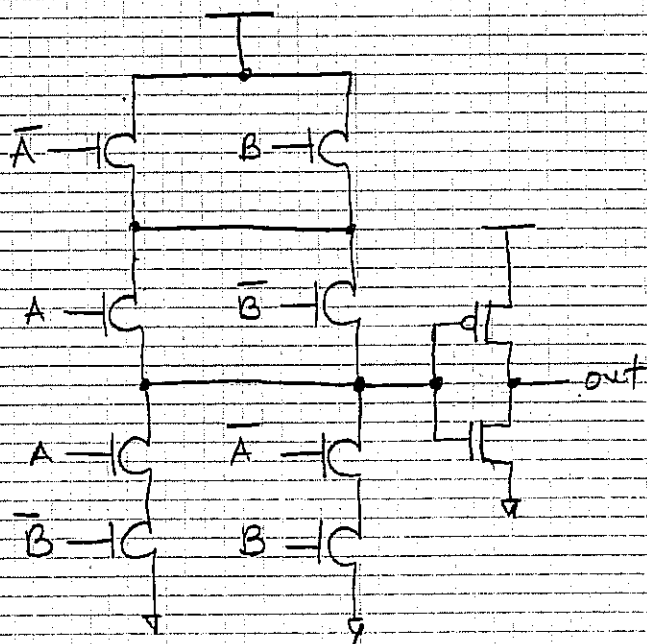

The following circuit is given:

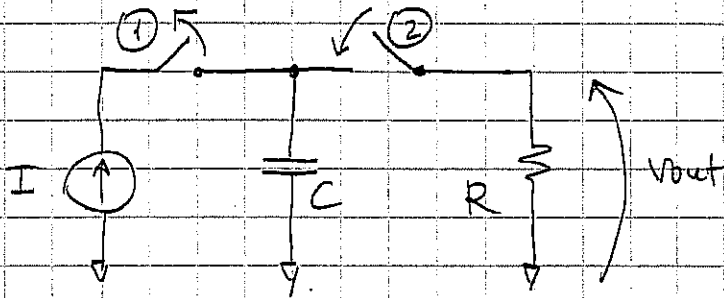


At  $t=0$  switch ① is closed switch ② is opened.

$t=\pi$  switch ① is opened switch ② closed.

Plot the waveform at  $v_{out}$  from  $t=0$  to  $t=\infty$ .

Switch (1) is closed & (2) is opened

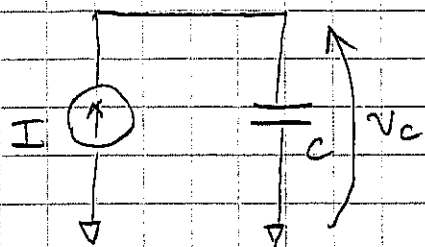


$$I = C \frac{dv_c}{dt}$$

$$v_c = \int_0^t \frac{I}{C} dt = \frac{I}{C} t$$

$$\text{At } t=T \quad v_c(T) = \frac{IT}{C}$$

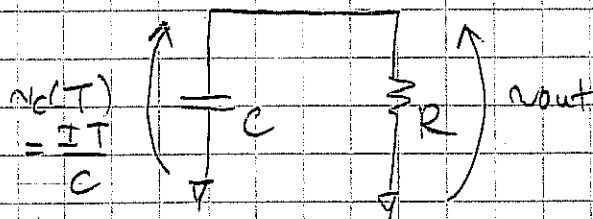
Now, at  $t=T$  switch (1) is opened & (2) is closed.




$$\text{Thus; } v_{out}(T) = v_c(T) = \frac{IT}{C}$$

$$v_{out}(t) = \frac{IT}{C} e^{-\frac{t}{RC}} \quad \text{for } t \geq T$$

The resultant waveform:

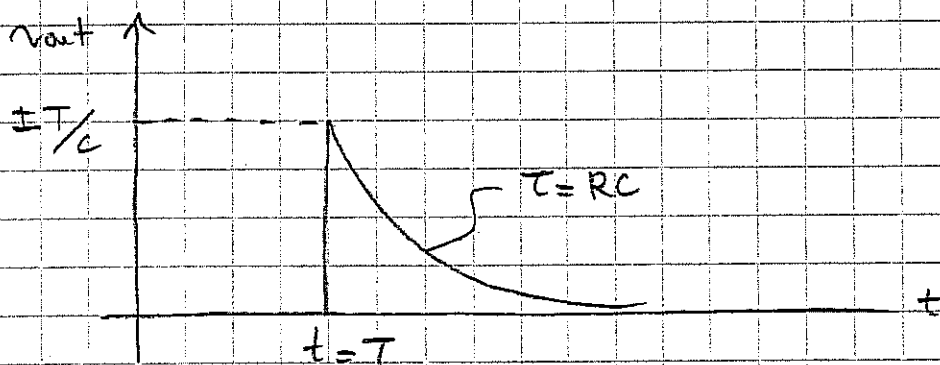



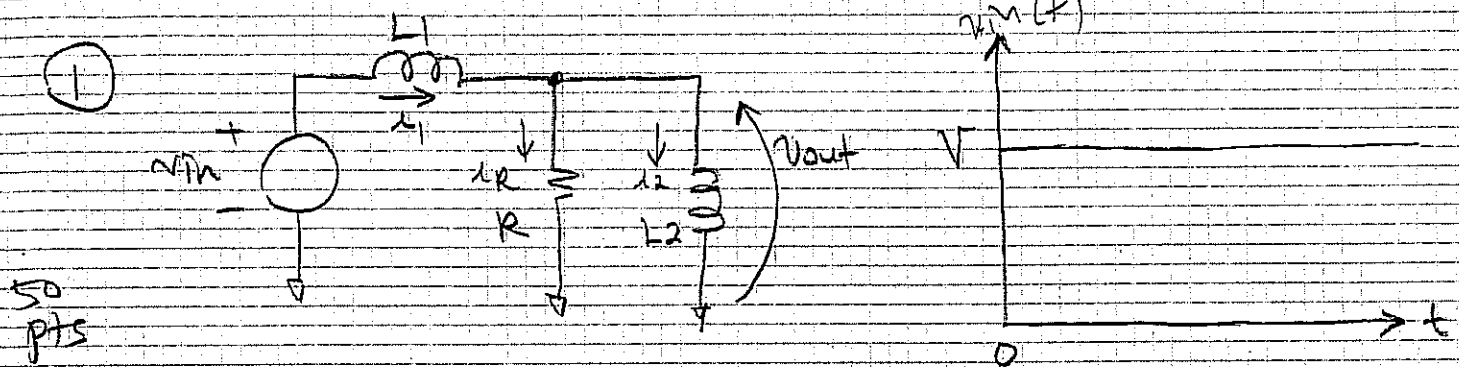

$$i_1(0) = 0 \text{ A} \quad \& \quad i_2(0) = 0 \text{ A}$$


find the expression for  $v_{out}$  only.

②  $out = ABC + D$

50 pts (a) Implement the output function above with CMOS

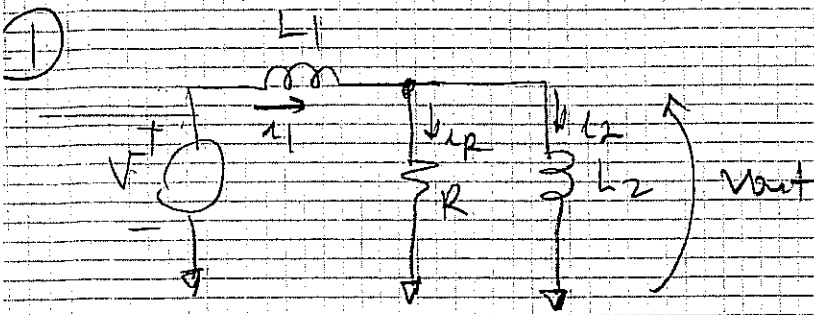(b) Find the transistor sizes for  $T_R = T_F = \tau_f$  if the minimum width is  $W$ .

NOTE = Do NOT use the output inverter in (a).



$$L_1 = L_1 + L_2 \quad (1)$$

$$V = V_{L1} + V_{out} = L_1 \frac{di_1}{dt} + R i_R \quad (2)$$

$$i_R R = L_2 \frac{di_2}{dt} \quad (3)$$

From (1)  $i_2 = i_1 - i_R$  substitute it to (3)

$$i_R R = L_2 \frac{d}{dt} (i_1 - i_R) = L_2 \frac{di_1}{dt} - L_2 \frac{di_R}{dt}$$

$$\frac{di_1}{dt} = \frac{1}{L_2} \left( i_R R + L_2 \frac{di_R}{dt} \right) \text{ substitute into (2)}$$

$$V = R i_R + \frac{L_1}{L_2} \left( i_R R + L_2 \frac{di_R}{dt} \right)$$

$$= R i_R + \frac{L_1}{L_2} R i_R + L_1 \frac{di_R}{dt}$$

$$\frac{di_R}{dt} + i_R \frac{R}{L_1} \left( 1 + \frac{L_1}{L_2} \right) = \frac{V}{L_1}$$

$$\text{Let } K \triangleq \frac{R}{L_1} \left( 1 + \frac{L_1}{L_2} \right) \Rightarrow \frac{di_R}{dt} + i_R K = \frac{V}{L_1}$$

General solution =

$$\frac{di_R}{dt} + K i_R = 0 \quad i_R = A e^{st} = A e^{-Kt}$$


particular solution =  $i_R = M$

Thus, substituting particular solution into the DE =

$$0 + M K = \frac{V}{L_1} \Rightarrow M = \frac{V}{K L_1}$$

$$i_R = A e^{-Kt} + \frac{V}{K L_1}$$

Initially =

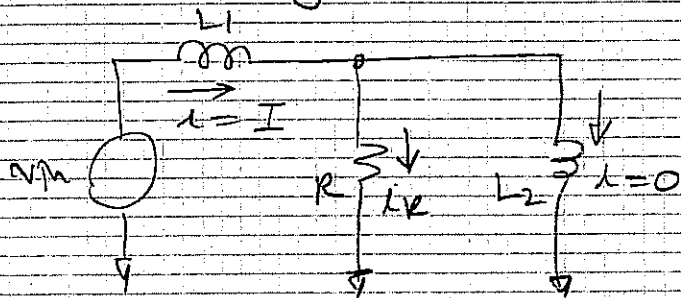

$$i_R(0) = 0 = A + \frac{V}{K L_1}$$

$$A = -\frac{V}{K L_1}$$


$$i_R = \frac{V}{K L_1} (1 - e^{-Kt}) = \frac{V}{\cancel{L_1} \frac{R}{\cancel{L_1}} (1 + \frac{L_1}{L_2})} \cdot \left[ 1 - e^{-\frac{R}{L_1} (1 + \frac{L_1}{L_2}) t} \right]$$

$$v_{out} = R i_R = \frac{V}{\left(1 + \frac{L_1}{L_2}\right)} \left[ 1 - e^{-\frac{R}{L_1} \left(1 + \frac{L_1}{L_2}\right) t} \right]$$

$$\Rightarrow v_{out} = \frac{V L_2}{(L_1 + L_2)} \left[ 1 - e^{-\frac{R}{L_1} \left(1 + \frac{L_1}{L_2}\right) t} \right]$$

$$(2) \quad \text{out} = \overline{A B C + D} = (\overline{A + B + C}) \overline{D}$$

(a)

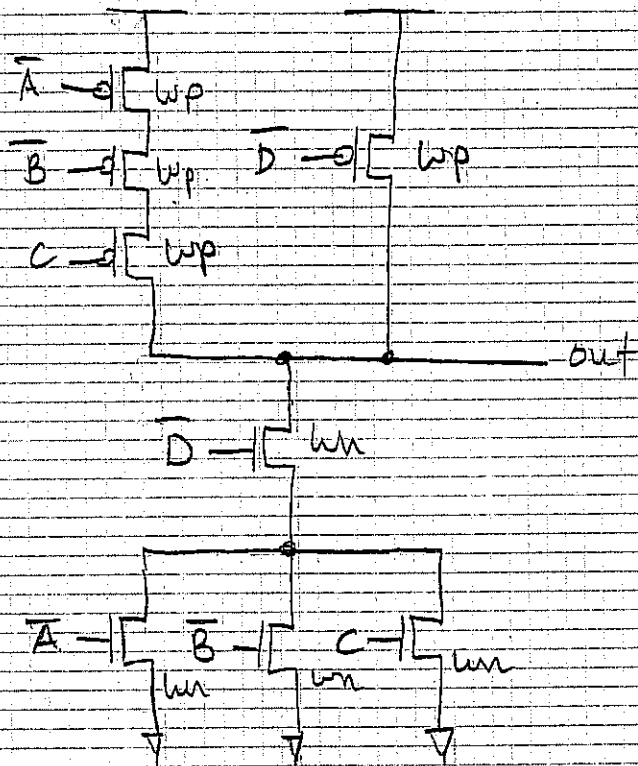

(b)

$$T_R = 2.2 R_{\text{eq}} C_L = 2.2 \times 3 \frac{K}{w_p} C_L$$

$$T_F = 2.2 R_{\text{eq}} C_L = 2.2 \times 2 \frac{K}{2w_n} C_L$$

$$T_R = T_F \Rightarrow \frac{3}{w_p} = \frac{1}{w_n} \Rightarrow w_p = 3w_n$$

$$\text{Let } w_n = w \Rightarrow w_p = 3w$$

The following function is given:


$$f = \overline{A} + \overline{B} \left[ \overline{C} + \overline{D} (\overline{E} + \overline{F}) \right]$$

This circuit needs to drive a large fan-out composed of a large capacitor, therefore, an inverter needs to be added to its output.

Implement the function,  $f$ , with minimum number of elements using transmission gate logic.

Since an inverter needs to be used at the output of  $f$ :
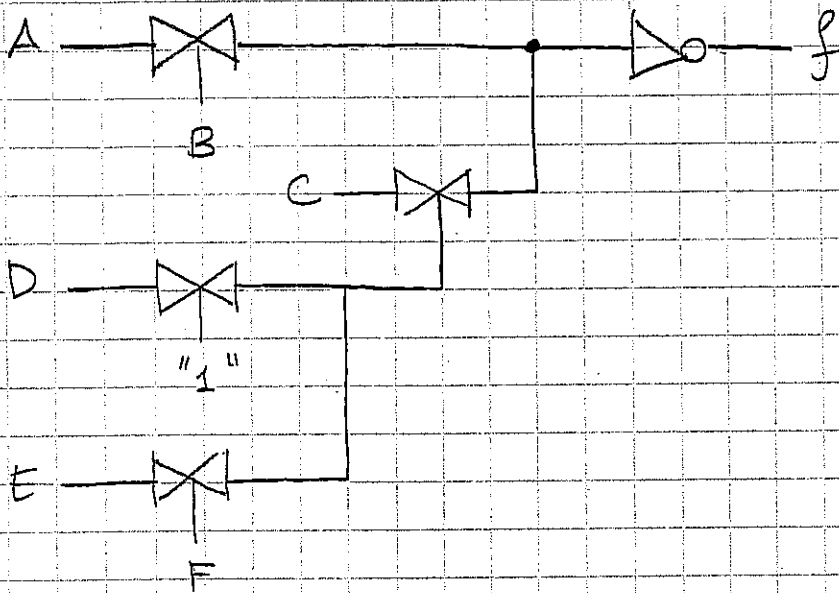
$$\begin{aligned} f &= \overline{(\overline{A} + \overline{B})} [\overline{C} + \overline{D}(E + \overline{F})] = \overline{(\overline{A} + \overline{B})} + [\overline{C} + \overline{D}(E + \overline{F})] \\ &= A B + C(D + E F) \end{aligned}$$



An inverter below is given.

$$V_{DD} = 3 \text{ V}$$


$$V_{TN} = V_{TP} = 0.6 \text{ V}$$

$$\text{Mobility for electrons } (\mu_n) = 1200 \text{ cm}^2/\text{Vsec}$$

$$\text{Mobility for holes } (\mu_p) = 600 \text{ cm}^2/\text{Vsec}$$

$$C_{OX} = 6.9 \times 10^{-7} \text{ F/cm}^2$$

$$L = 0.25 \text{ } \mu\text{m}$$

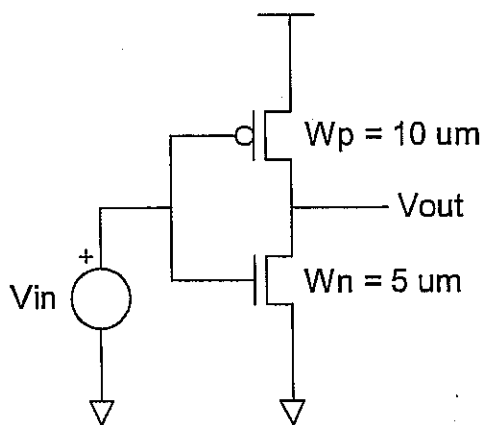

The current through a MOSFET is defined as:

$$I_D = \frac{\mu C_{OX} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


- (a) Compute the static DC current when  $V_{in} = 2 \text{ V}$  ( $C_{OUT} = 0 \text{ F}$ ).
- (b) Compute the output voltage when  $V_{in} = 2 \text{ V}$ .

HINT: Consider the equivalent circuits of nfet and pfet at this bias condition.

For  $V_{in} = 2V \Rightarrow$  nfet is in linear region

p fet is in saturation region.

Eq. circuit =

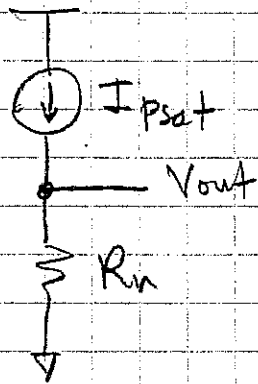

$$\begin{aligned} I_{psat} &= \frac{\mu_p C_{ox} W_p}{2L} (V_{sgp} - V_T)^2 \\ &= \frac{600 \times 6.9 \times 10^{-7} \times 10}{2 \times 0.25} (1 - 0.6)^2 \\ &= 1.32 \text{ mA} \end{aligned}$$

For nfet  $I_D \approx \frac{\mu_n C_{ox} W}{L} (V_{gsn} - V_T) V_{dsn} = I_{psat}$

$$= \frac{1200 \times 6.9 \times 10^{-7} \times 5}{0.25} (2 - 0.6) V_{out} = 1.32 \times 10^{-3}$$

$$V_{out} = \frac{1.32 \times 10^{-3}}{0.023} = 57 \text{ mV}$$



(1)

$$sum = A \oplus B \oplus Cin$$

$$Cout = AB + Cin(A + B)$$

(a) Draw the schematic in CMOS implementing sum and Cout. Assume to use an output inverter due to high load capacitance, CL.

(b) Draw the schematic in transmission gates implementing sum and Cout. Also use an output inverter due to high load capacitance, CL.

(2)

(a) Obtain only the pfet tree for the following function,

$$out = \overline{E} + \overline{D}(\overline{A} + \overline{BC})$$


(b) Now construct the nfet tree separately from the pfet tree obtained in (a), yielding the same function, out.


(c) Now join the nfet and pfet trees and size them according to  $R_{inv} = 4$  (inverter ratio) in units of W. The minimum width must be W/2 in the schematic.

(d) Find TR/TF (the ratio of rise time to fall time).


(3)

Find  $V_x$  after the switch closes.

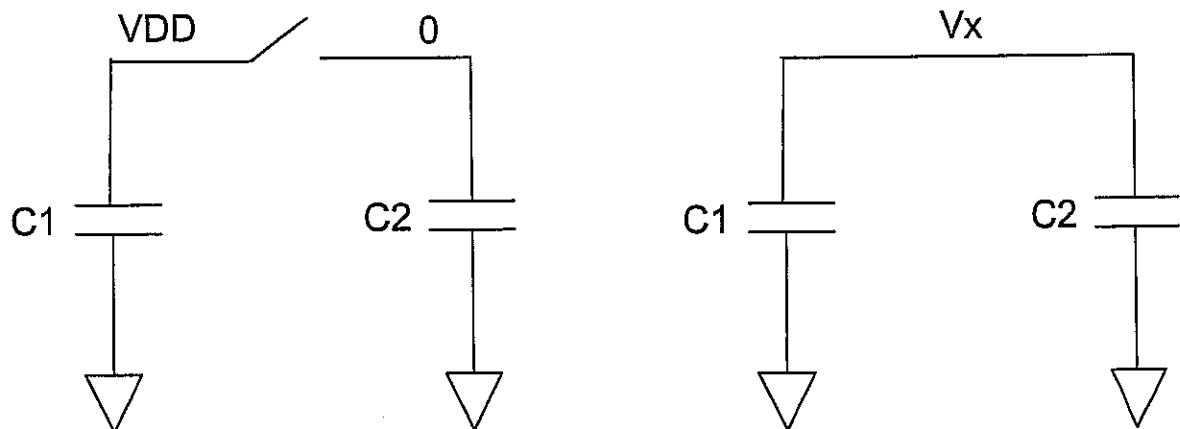

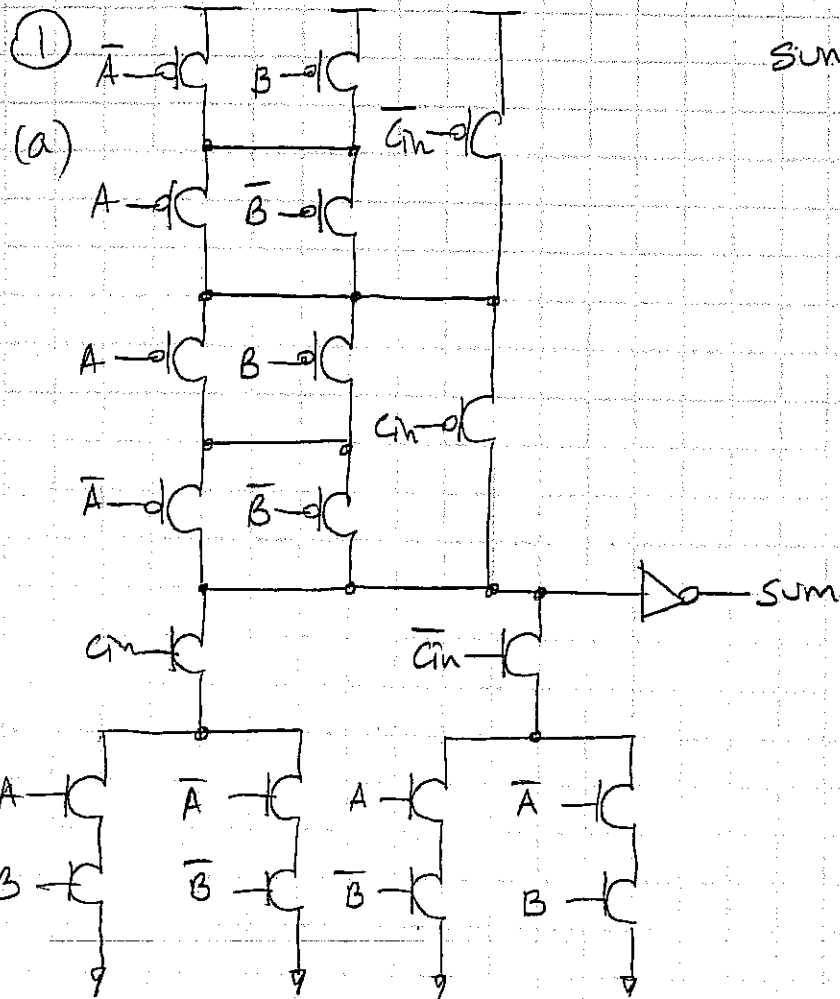
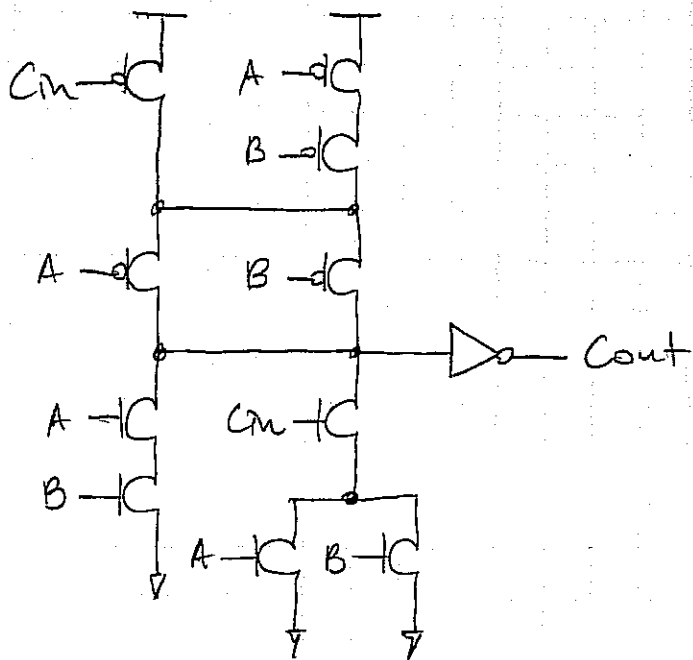
$$\begin{aligned} \text{Sum} &= A \oplus B \oplus C = (A\bar{B} + \bar{A}B) \oplus C \\ &= (A\bar{B} + \bar{A}B) C + (A\bar{B} + \bar{A}B) \bar{C} \\ &= (\bar{A}\bar{B} + AB) C + (A\bar{B} + \bar{A}B) \bar{C} \end{aligned}$$



$$\text{Cout} = AB + C(A + B)$$

$$(b) \text{ Sum} = \overline{\overline{A \oplus B \oplus C}} = \overline{(\overline{A}B + A\overline{B}) \oplus C}$$

$$= (\overline{A}B + A\overline{B}) \overline{C} + (A\overline{B} + \overline{A}B)C$$


$$= [(\overline{A}B + A\overline{B}) + C][(\overline{A}B + A\overline{B}) + \overline{C}]$$

$$= (\overline{A}B + A\overline{B})(\overline{A}B + A\overline{B}) + \overline{C}(\overline{A}B + A\overline{B}) + C(\overline{A}B + A\overline{B})$$


$$= \overline{C}(\overline{A}B + A\overline{B}) + C(\overline{A}B + A\overline{B})$$

$$\text{Cout} = \overline{A \oplus B \oplus C} = \overline{(\overline{A} + B)(\overline{C} + A\overline{B})} = \overline{\overline{C}(\overline{A} + B) + A\overline{B}}$$
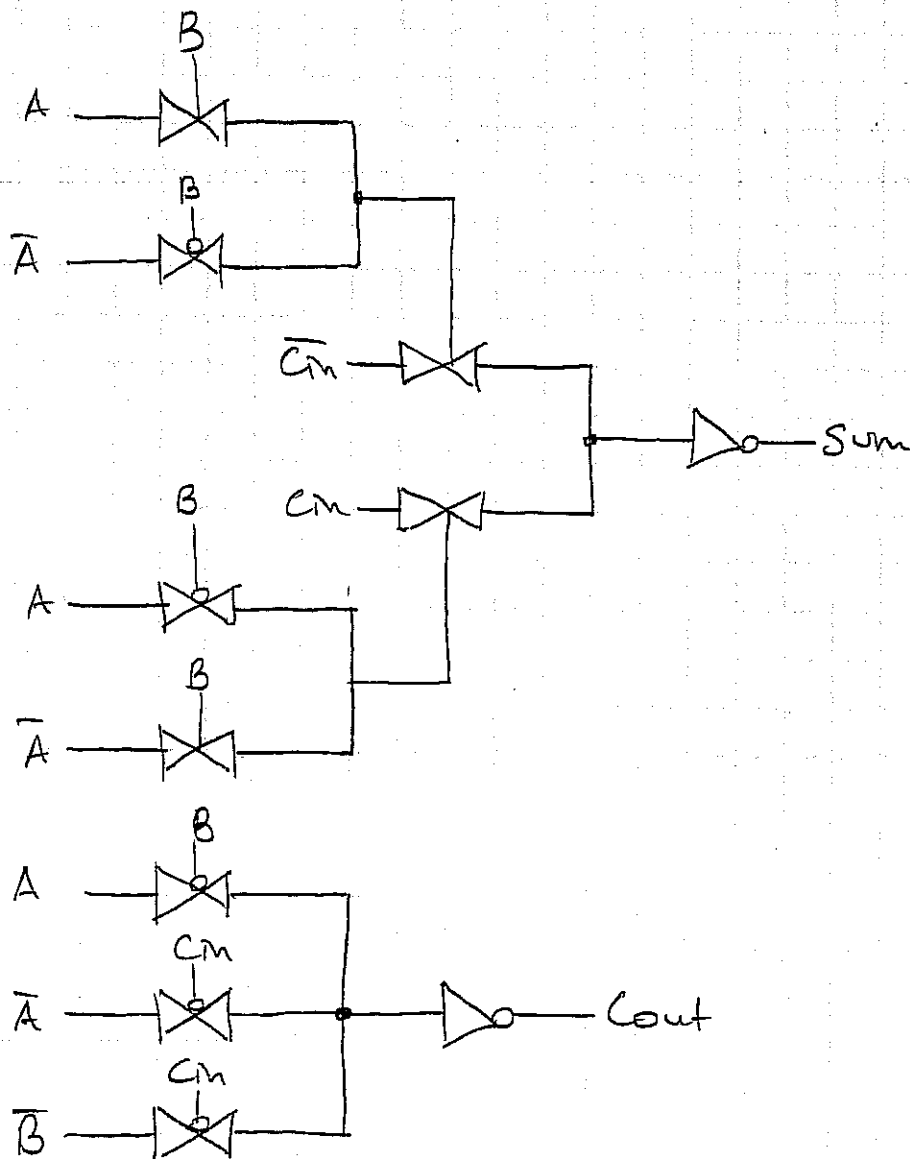
$$= \overline{\overline{C}A + \overline{C}B + A\overline{B}}$$




② (a)

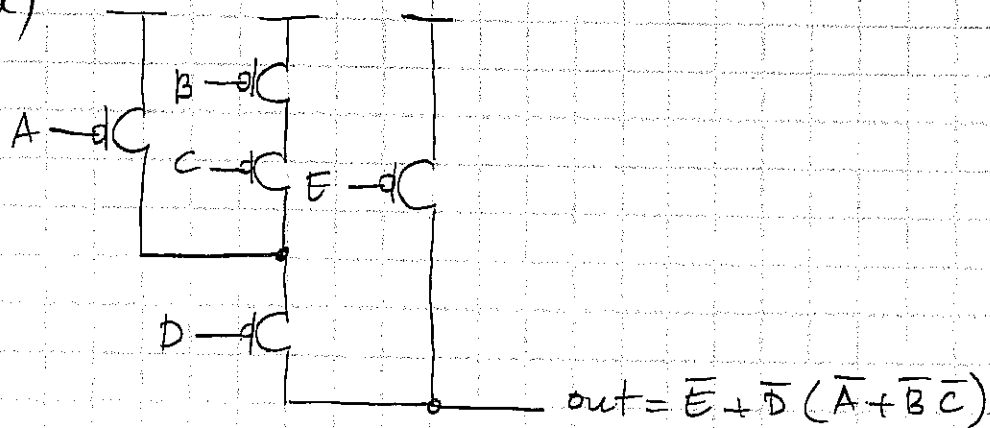


(b) Since  $out = \bar{E} + \bar{D}(\bar{A} + \bar{B}\bar{C})$

$$out = \overline{E \{ D + [A(B+C)] \}} = E [D + A(B+C)]$$

Thus, the n fct tree:

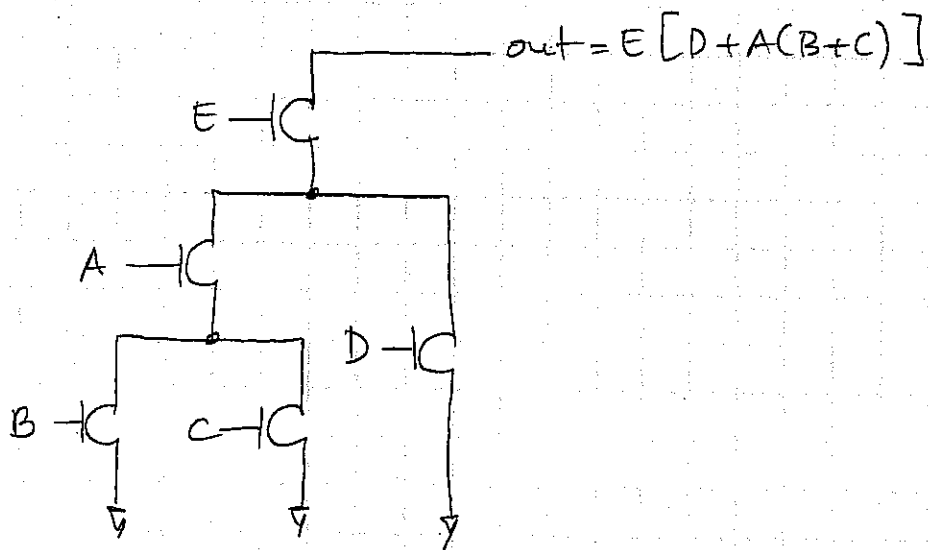

(c)

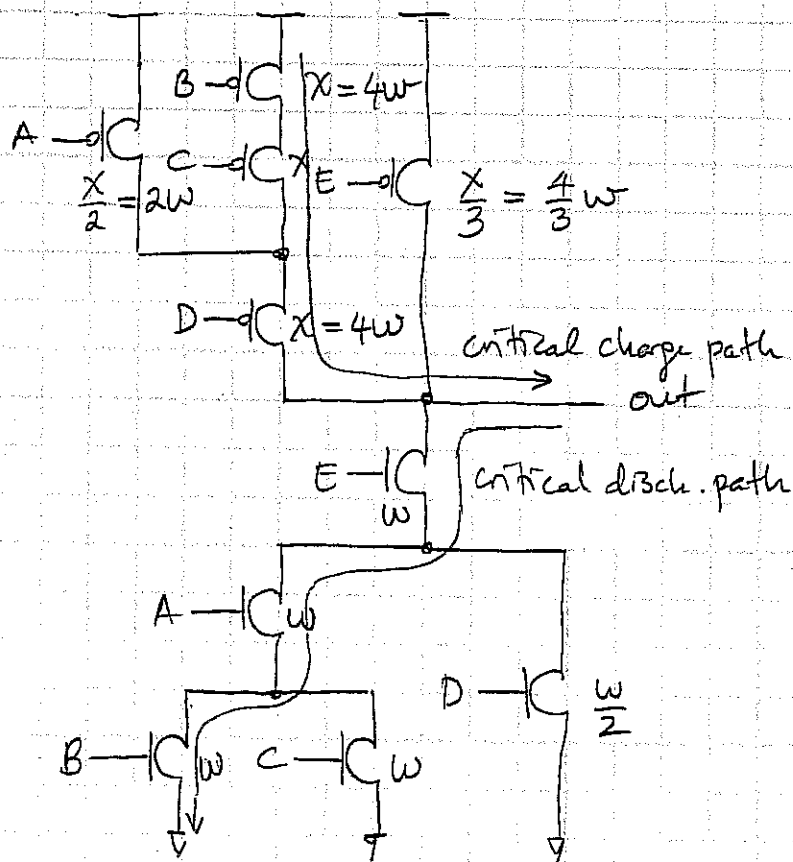


$$R_{eq} = \frac{K}{2w} \times 3 = \frac{K}{2(\frac{w}{3})} \Rightarrow w_{eq} = \frac{w}{3}$$

$$R_{eq} = \frac{K}{X} \times 3 = \frac{K}{(\frac{X}{3})} \Rightarrow w_{eq} = \frac{X}{3}$$


$$\text{Since } R_{no} = 4 = \frac{w_{eq}}{w_{eq}} \Rightarrow 4 = \frac{X}{3} \cdot \frac{3}{w} \Rightarrow X = 4w$$

$$\left. \begin{aligned} (d) \quad T_R &= 2.22 C_L \frac{K}{4w} \times 3 \\ T_F &= 2.22 C_L \frac{K}{2w} \times 3 \end{aligned} \right\} \quad T_R/T_F = \frac{1}{4w} \cdot 2w = 0.5$$

(3)

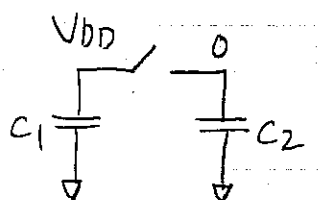

$$Q_{total}^{before} = C_1 V_{DD}$$

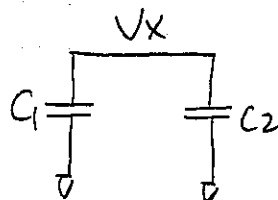

$$Q_{total}^{after} = (C_1 + C_2) V_X$$

$$Q_{total}^{before} = Q_{total}^{after}$$

$$C_1 V_{DD} = (C_1 + C_2) V_X$$


$$V_X = \frac{C_1}{(C_1 + C_2)} V_{DD}$$

Implement the following function using CMOS.

$$out = (A + \overline{BC})(D + E)$$

- (a) Implement this function with an inverter at the output. Size the transistors such that the inverter ratio,  $R_i$ , is equal to 1. Use  $W$  as the minimum width.
- (b) Implement the same function without an output inverter. Size the transistors such that  $TR = 2 TF$ . Use  $W$  as the minimum NMOS transistor width (PMOS width can be smaller).
- $TR = 2.22 CL R_{peq}$   
 $TF = 2.22 CL R_{neq}$   
 $CL$  is the output load capacitor  $R_{peq}$  and  $R_{neq}$  are the equivalent resistors in the charge and discharge paths, respectively.  
Ignore the intrinsic capacitances and the resulting Elmore's effect.

(a)

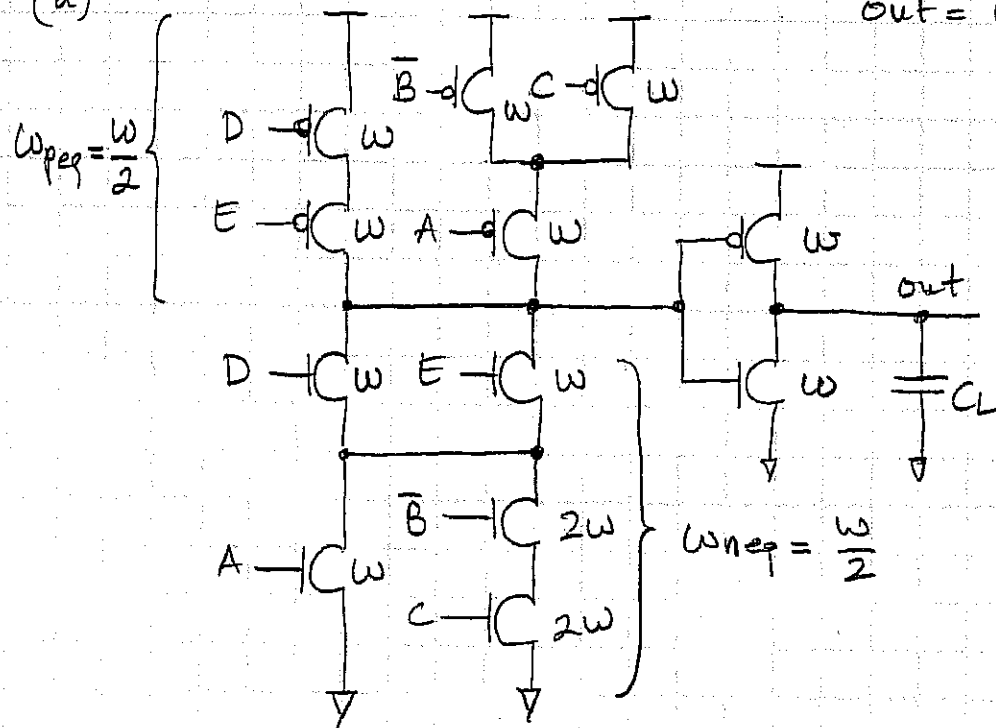

$$\text{out} = (A + \bar{B}C)(D + E)$$

$$R_i = \frac{\omega_{peg}}{\omega_{neg}} = \frac{\omega/2}{\omega/2} = 1$$

$$(b) \quad \text{out} = \overline{(A + \bar{B}C)(D + E)} = \overline{\bar{A}(B + \bar{C}) + \bar{D}\bar{E}}$$

$$T_F = 2.22 C_L 2 R_n = 2.22 C_L 2 \frac{K}{2 \omega_n}$$

$$T_R = 2.22 C_L 3 R_p = 2.22 C_L 3 \frac{K}{\omega_p}$$

$$T_R = 2 T_F \Rightarrow \frac{3}{\omega_p} = 2 \frac{1}{\omega_n}$$

$$\omega_p = \frac{3}{2} \omega_n \quad \text{Let } \omega_n = \omega$$

$$\text{Then; } \omega_p = \frac{3\omega}{2}$$

