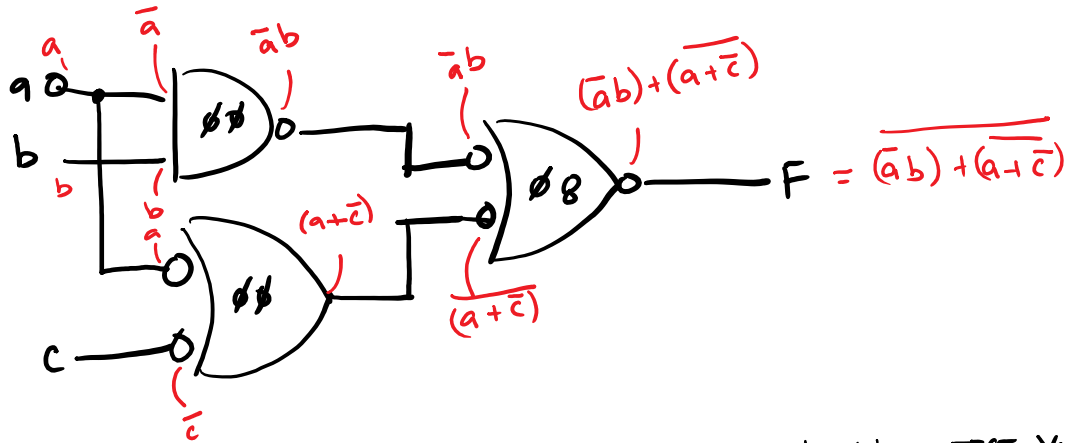


Practice Problems 1 Solutions

Tuesday, September 13, 2016 3:24 PM

FIND THE EQUATION:




ASSUMPTIONS:

A IS ACTIVE LOW

B, C, F ARE ACTIVE HIGH

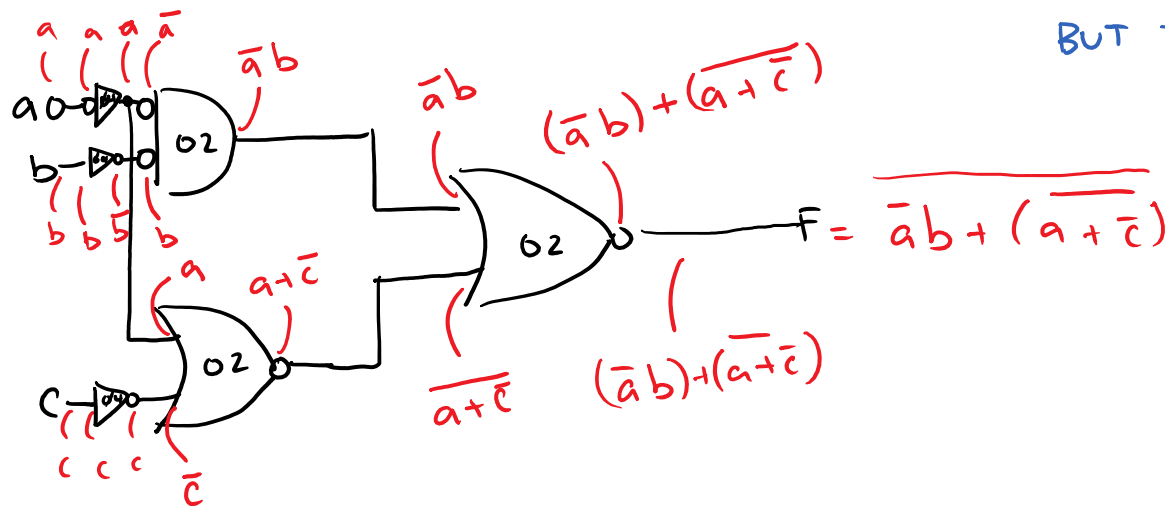REDESIGN THE CIRCUIT USING ONLY 2'S & 4'S. TEST YOUR CIRCUIT



BUT THERE'S A BETTER DESIGN!

Practice Problems 1 Solutions

Thursday, September 15, 2016


5:21 PM

	A	B	C	F
6	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$\begin{aligned}
 F &= (\bar{a}b) + (a + \bar{c}) \\
 &= (\bar{a}b) + \bar{a} + \bar{c} \\
 &= \bar{a}b + \bar{a} + \bar{c} \\
 &= \bar{a}b + \bar{a} + \bar{c} \\
 &= (a + \bar{b})(a + \bar{c}) \\
 &= a + a\bar{c} + a\bar{b} + \bar{b}\bar{c} \\
 &= a(b + \bar{b})(c + \bar{c}) + a\bar{c}(b + \bar{b}) + a\bar{b}(c + \bar{c}) + \bar{b}\bar{c}(a + \bar{a}) \\
 &= (ab + a\bar{b})(c + \bar{c}) + a\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}\bar{c} \\
 &= abc + ab\bar{c} + a\bar{b}c + a\bar{b}\bar{c} + \cancel{abc} + \cancel{ab\bar{c}} + \cancel{a\bar{b}c} + \cancel{a\bar{b}\bar{c}} + \cancel{abc} + \cancel{ab\bar{c}} + \cancel{a\bar{b}c} + \cancel{a\bar{b}\bar{c}} + \bar{a}\bar{b}\bar{c} \\
 &= abc + ab\bar{c} + a\bar{b}c + a\bar{b}\bar{c} + \bar{a}\bar{b}\bar{c} \quad (\text{CANONICAL FORM})
 \end{aligned}$$

BC	00	01	11	10
A	0	1	1	0
B	0	0	1	1
C	0	1	0	0
F	1	0	0	1
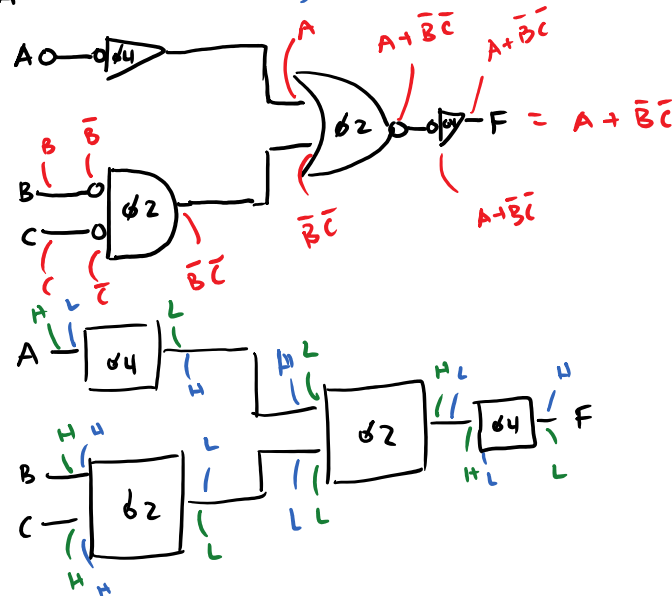
$$F = A + \bar{B}\bar{C} \quad (\text{SIMPLIFIED})$$




Practice Problems 1 Solutions


Thursday, September 15, 2016 4:24 PM

FIND THE EQUATION


CHANGE PART #

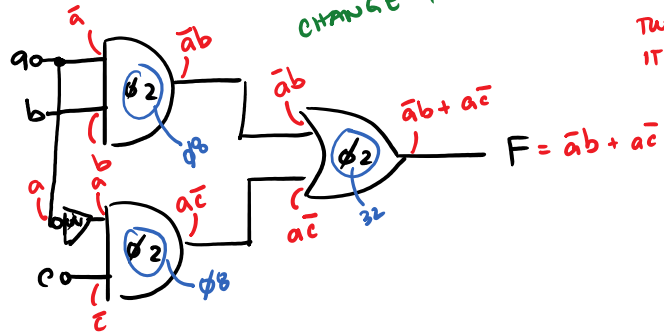

USE PART #2 AND FIX THE BUBBLES

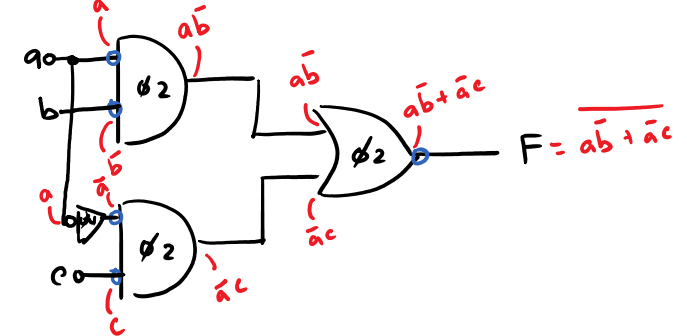

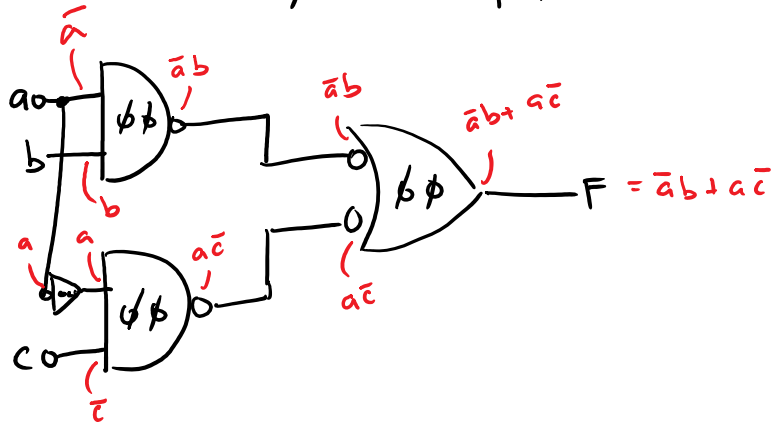REDO WITH ONLY $\phi\phi$'s $\neq \phi4$'s. TEST YOUR CIRCUIT



ASSUMPTIONS:
A, C ARE ACTIVE LOW
B, F ARE ACTIVE HIGH
 $F = \bar{a}b + a\bar{c}$ IS
WHAT THE CUSTOMER
WANTED

Practice Problems 1 Solutions


Friday, September 16, 2016 11:55 AM

A	B	C	F
0	0	0	0
1	0	1	0
2	0	1	1
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	0

$$\begin{aligned}
 F &= \bar{a}b + a\bar{c} \\
 &= \bar{a}b(c + \bar{c}) + a\bar{c}(b + \bar{b}) \\
 &= \bar{a}bc + \bar{a}b\bar{c} + ab\bar{c} + a\bar{b}\bar{c}
 \end{aligned}$$


A \ Bc	00	01	10	11
00	0	0	0	0
01	0	1	0	0
10	0	0	1	0
11	0	0	0	1

$$F = \bar{a}b + a\bar{c} + b\bar{c}$$

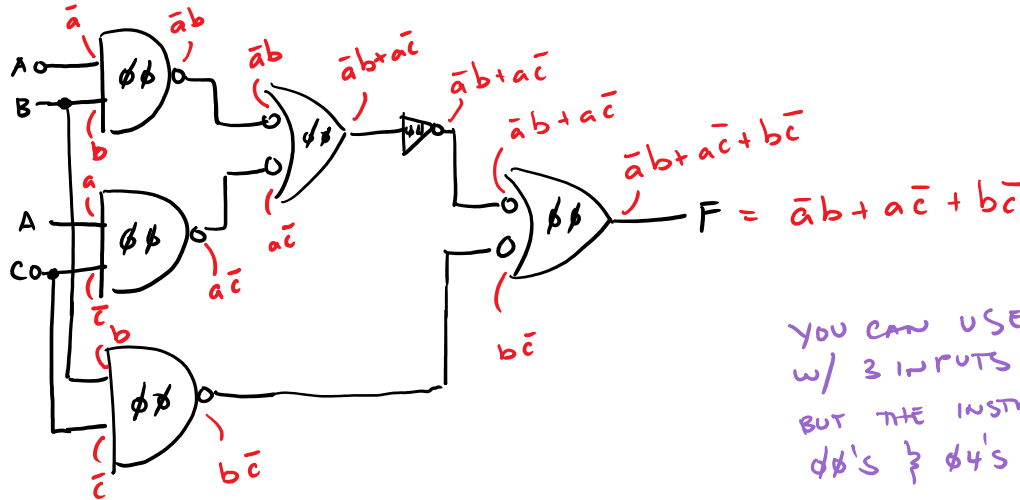

YOU CAN USE AN OR FUNCTION
w/ 3 INPUTS HERE INSTEAD
BUT THE INSTRUCTIONS SAY TO USE
 $\phi\phi$ 'S & $\phi\phi$ 'S

--	++	--	++
A	B	C	F
0	H	L	H
1	H	L	L
2	H	H	H
3	H	H	L
4	L	L	H
5	L	L	L
6	L	H	H
7	L	H	L

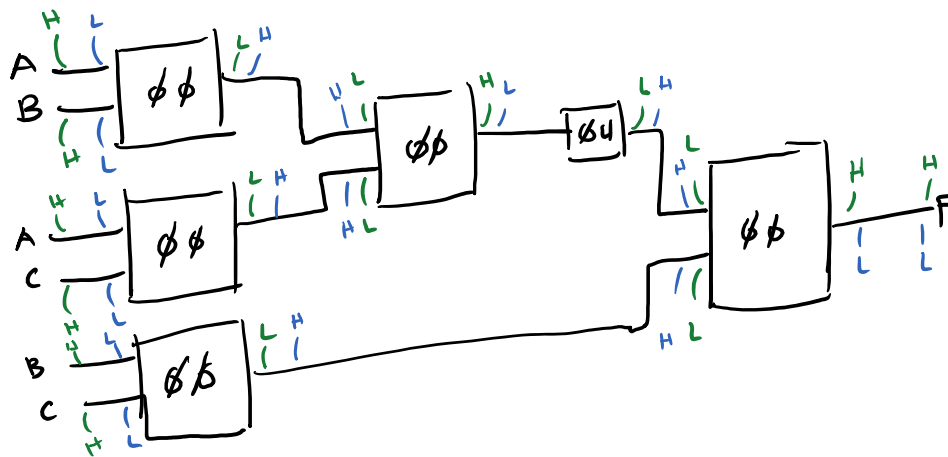

Practice Problems 1 Solutions

Thursday, September 15, 2016 4:55 PM

DESIGN A CIRCUIT THAT CAN DETECT BCD (BINARY CODED DECIMAL)

	B ₃	B ₂	B ₁	B ₀	F
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

NOT BCD

	B ₃	B ₂	B ₁	B ₀	F
0	L	L	L	L	L
1	L	L	L	H	L
2	L	L	H	L	L
3	L	L	H	H	L
4	L	H	L	L	L
5	L	H	L	H	L
6	L	H	H	L	L
7	L	H	H	H	L
8	H	L	L	L	L
9	H	L	L	H	L
10	H	L	H	L	L
11	H	L	H	H	L

B ₃ B ₂	00	01	11	10
B ₁ B ₀	00 0 4 12 8	01 1 5 13 9	11 3 7 15 11	10 2 6 14 10

$$F = \bar{B}_3 + \bar{B}_2 \bar{B}_1$$

ASSUMPTIONS:
B_{3,2,1,0} ARE ACTIVE HIGH
F IS ACTIVE LOW
CHALLENGE: ONLY USE 32 & φ8

