

Review Session II

Friday, October 21, 2016 11:21 AM

$$F = Q_1 Q_0 A B D + \overline{Q_1} \overline{Q_0} ((+B) D)$$

D is control

use a (153)

