
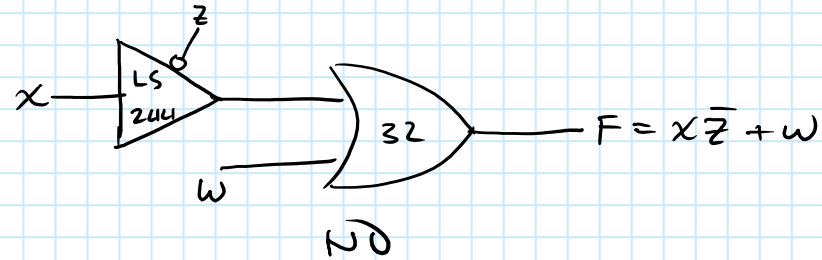



Hi-Z Device

Tuesday, November 15, 2016 8:35 AM

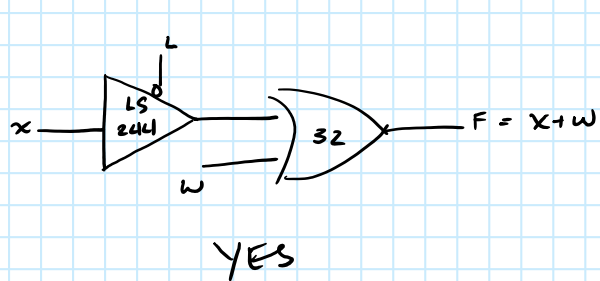

TRUTH TABLE

Z	A	F
0	-	HiZ
1	0	0
1	1	1

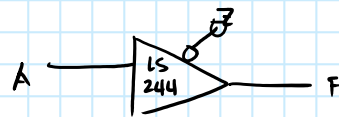

If $z = 0$ or H (because the enable is active low), then the output of the LS244 is HiZ.
If you attach this input to a device, it acts like there was no input at all.

