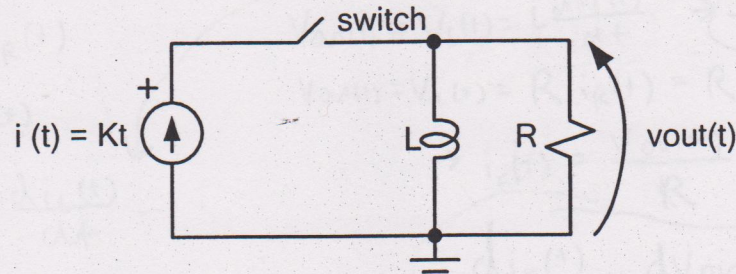


Question 1 (50 points):

The following circuit is given:




1	25
2	25
T	50

In this circuit, the switch is closed at $t = 0$ sec. The input current is linearly varying with time, $i(t) = Kt$, with a slope of K (a constant value) as shown.


Assuming that the current stored in the inductor, $i_L(0) = 0$ A. Find the expression for $v_{out}(t)$ and plot it using **time-domain analysis** (diff equation method).

Question 2 (50 points):

The following circuit is given:

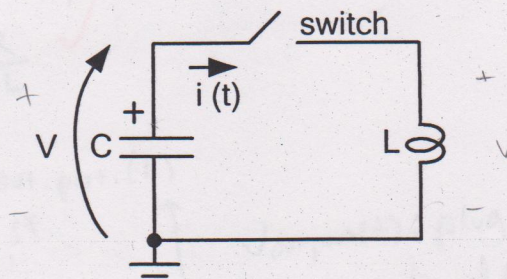

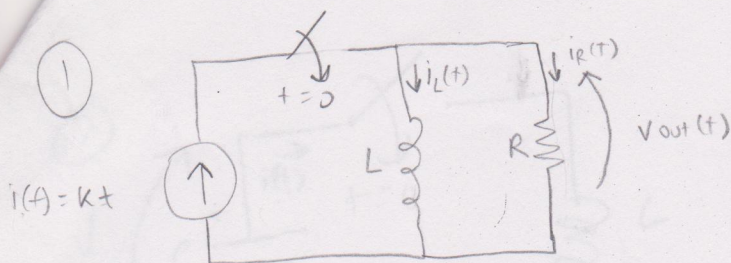In this circuit, the switch is closed at $t = 0$ sec. Assuming the voltage across the capacitor at $t = 0$ sec, is 0 V at the direction shown in the figure, determine the expression for current, $i(t)$, the voltage across the inductor, $v_L(t)$, the voltage across the capacitor, $v_C(t)$ using **time-domain analysis**. Plot each waveform.



$$i_L(0) = 0A$$

Find $V_{out}(t)$

$$i(t) = i_L(t) + i_R(t)$$

$$i_R(t) = i(t) - i_L(t)$$

$$\frac{di_R(t)}{dt} = \frac{di(t)}{dt} - \frac{di_L(t)}{dt}$$

$$V_{out}(t) = V_L(t) = L \frac{di_L(t)}{dt} \Rightarrow \frac{di_L(t)}{dt} = \frac{V_{out}(t)}{L}$$

$$V_{out}(t) = V_L(t) = R \cdot i_R(t) = R(i(t) - i_L(t))$$

$$\Rightarrow i_R(t) = \frac{V_{out}(t)}{R}$$

$$\frac{di_R(t)}{dt} = \frac{dV_{out}(t)}{R}$$

$$\frac{1}{R} \frac{dV_{out}(t)}{dt} = K - \frac{V_{out}(t)}{L}$$

$$\left(\frac{1}{R} \frac{dV_{out}(t)}{dt} + \frac{1}{L} V_{out}(t) = K \right)$$

$$\frac{s}{R} + \frac{1}{L} = 0 \Rightarrow s = -\frac{R}{L}$$

$$V_{out}(t) = V_{out, gen.}(t) + V_{out, part.}(t)$$

$$V_{out, gen.}(t) = A e^{st}$$

$$V_{out}(t) = A e^{st} - \frac{L}{R}$$

@ $t=0$:

$$V_{out}(0) = A - \frac{L}{R} = 0$$


$$A = \frac{L}{R}$$


$$V_{out}(t) = \frac{L}{R} \left(e^{-\frac{Rt}{L}} \right)$$

$V_{out, part.}(t)$: plug K into dif. eq:

$$\frac{1}{R} \cdot \frac{d(K)}{dt} + \frac{1}{L} (K) = 0$$
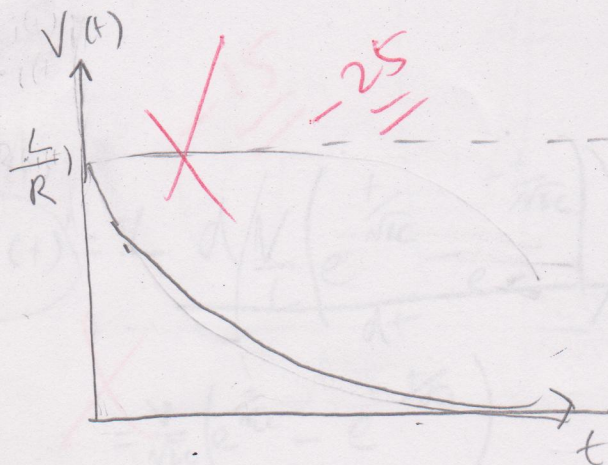
$$-\frac{1}{R} = \frac{1}{L} K \Rightarrow K = -\frac{L}{R}$$



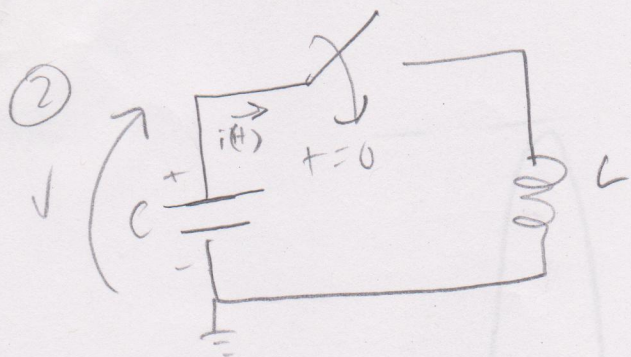

$$V_c(0) = 0$$

Find $i(t)$, $V_c(t)$, $V_L(t)$

$$V_c'(t) = V_L(t)$$

$$-i_c(t) = i(t) = i_L(t)$$

$$\frac{1}{LC} \left(\frac{d^2 i_L(t)}{dt^2} + i_c(t) \right) = 0$$

$$\frac{d^2 i_L(t)}{dt^2} + \frac{i_L(t)}{LC} = 0$$

$$s^2 = -\frac{1}{LC} \quad \alpha = 0 \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

$$s = \pm j\sqrt{\frac{1}{LC}}$$

$$i(t) = A e^{s_1 t} + B e^{s_2 t} + 0$$

$$i(0) = 0 = A + B \rightarrow B = -A$$

$$\frac{di(0)}{dt} = s_1 A e^{s_1 t} + s_2 B e^{s_2 t}$$

$$= s_1 A + s_2 B = \frac{V_L}{L}$$

$$= s_1 A - s_2 A = \frac{V_L}{L}$$

$$= A(s_1 - s_2) = \frac{V_L}{L}$$


$$A = \frac{V_L}{L}$$

$$i(t) = \frac{V}{L} \left(e^{+j\sqrt{\frac{1}{LC}}t} - e^{-j\sqrt{\frac{1}{LC}}t} \right)$$

$$V_L(t) = V_c(t) = L \frac{d}{dt} \left(\frac{V}{L} \left(e^{+j\sqrt{\frac{1}{LC}}t} - e^{-j\sqrt{\frac{1}{LC}}t} \right) \right)$$

$$= \frac{V}{\sqrt{LC}} \left(e^{+j\sqrt{\frac{1}{LC}}t} - e^{-j\sqrt{\frac{1}{LC}}t} \right)$$

Waveforms on next page

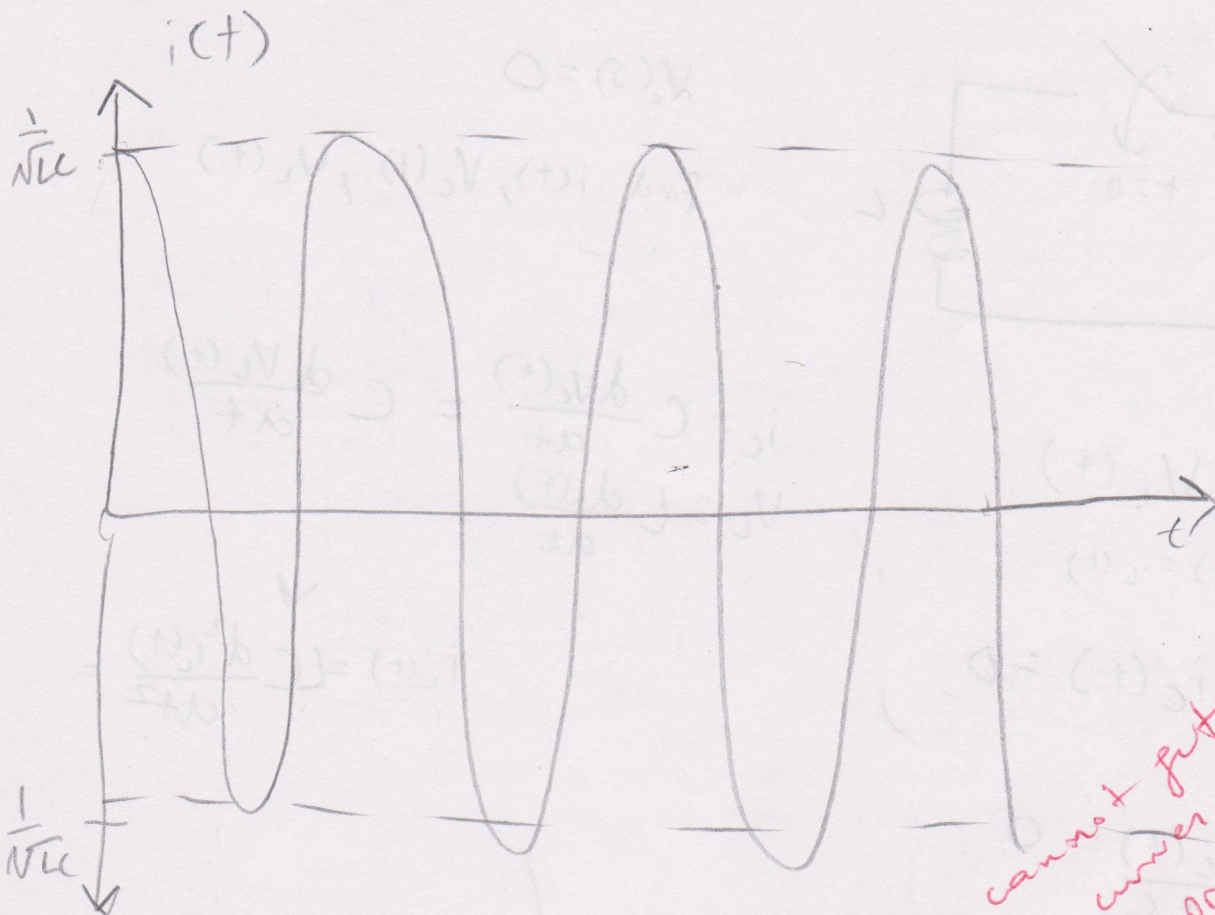

you cannot get
your answer from
your expressions!

$$\frac{10}{\sqrt{LC}} = 2$$

