

Last Name _____

First Name _____

IMPORTANT REMINDERS: You Must show all your work, Must use Mix Logic notations, Write all your assumptions, TTL Manual is not a notebook! All given circuits uses the mix logic notations.

1. Perform the following arithmetic operation in binary using 2's complement representation. You have 7 bits to work. **Must show your work.**

$$Y = -25_{10} - 46_{10}$$

$$25 = 0011001$$

$$-25 = 1100110 \rightarrow \text{one's complement}$$

$$\begin{array}{r} \text{Two's complement} = 1100110 \\ +1 \\ \hline 1100111 \end{array}$$

$$46 = 0101110$$

$$-46 = 1010001 \rightarrow \text{one's complement}$$

$$\begin{array}{r} \text{Two's complement} \\ 1010001 \\ +1 \\ \hline 1010010 \end{array}$$

$$\text{Adding } (-25) + (-46)$$

$$\begin{array}{r} 1100111 \\ + 1010010 \\ \hline 1011001 \end{array}$$

Discarded

$$\begin{array}{r} 65 \ 4 \ 3 \ 2 \ 1 \ 0 \\ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \\ 0 \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \end{array}$$

$$\begin{array}{r} -25 \\ -46 \\ \hline -71 \end{array}$$

$$\text{checking } 1000110$$

$$\begin{array}{r} 1000110 \\ +1 \\ \hline 1000111 \end{array}$$

not enough bits

Wrong ans

2. Convert the following number: **Must show your work.**

354₈

a) to Binary 011101100 \rightarrow From the table on scratch paper

b) to Hex $011101100 = EC_{16}$

c) to Decimal $(3 \times 8^2) + (5 \times 8) + (4 \times 8^0) = 3 \times 64 + 40 + 4 = 236_{10}$

3. In Figure 1 what is the capacitor charging current (I_c) for 2 time constant after the switch is closed. The capacitor has initially 0 charge.

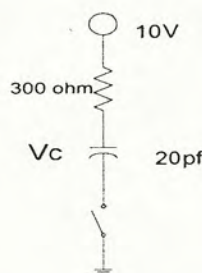


Figure 1.

$$t = 2$$

$$t = 2RC$$

$$RC = 300 \times 20 \times 10^{-12}$$

$$V_c = V_{cc} [1 - e^{-t/RC}]$$

$$V_c = 10 [1 - e^{-2/6 \times 10^{-9}}]$$

$$\frac{V_c}{10} - 1 = -e^{-2/6 \times 10^{-9}}$$

$$1 - \frac{V_c}{10} = e^{-2/6 \times 10^{-9}}$$

$$\ln(1 - \frac{V_c}{10}) = -2/6 \times 10^{-9}$$

$$\ln(1 - \frac{V_c}{10}) = -0.33 \times 10^9$$

$$-\ln(1 - \frac{V_c}{10}) = 0.33 \times 10^9$$

$$\ln(1 - \frac{V_c}{10}) = -0.33 \times 10^9$$

$$1 - \frac{V_c}{10} = e^{-0.33 \times 10^9}$$

$$1 - \frac{V_c}{10} = 0.7170676488$$

$$\frac{V_c}{10} = 0.2829323512$$

$$V_c = 2.829323512$$

$$I_c = \frac{V_c}{RC}$$

$$I_c = \frac{2.829323512}{300 \times 20 \times 10^{-12}}$$

$$I_c = 4.715539187 \times 10^{-12} \text{ A}$$

$$I_c = \frac{V_c}{RC}$$

$$= \frac{71706764.88}{300 \times 20 \times 10^{-12}}$$

$$= 11951 \times 10^{12} \text{ A}$$

What is this?

$$V_c = 71706764.88 \text{ V}$$

Design the given equation:

a) Using only 7402 and 7404. Do not change the equation

12

$$F = X \cdot Y + Z \cdot (X + Y)$$

X MSB AND Z LSB.

Z is negative assigned

XY and F are positive assigned


5 b) The output of the circuit should turn a LED on whenever it is true.

LED $I_d = 10\text{mA}$, $V_d = 1.6\text{V}$


Data for 7402

$V_{CC} = 5$	$V_{OH} = 2.4\text{V}$
$V_{IH} = 2\text{V}$	$V_{OL} = 0.4\text{V}$
$V_{IL} = 0.8\text{V}$	$I_{OH} = -0.4\text{mA}$
$I_{IH} = 40\mu\text{A}$	$I_{OL} = 16\text{mA}$
$I_{IL} = -16\mu\text{A}$	

10 c) Test your circuit for minterm 3.

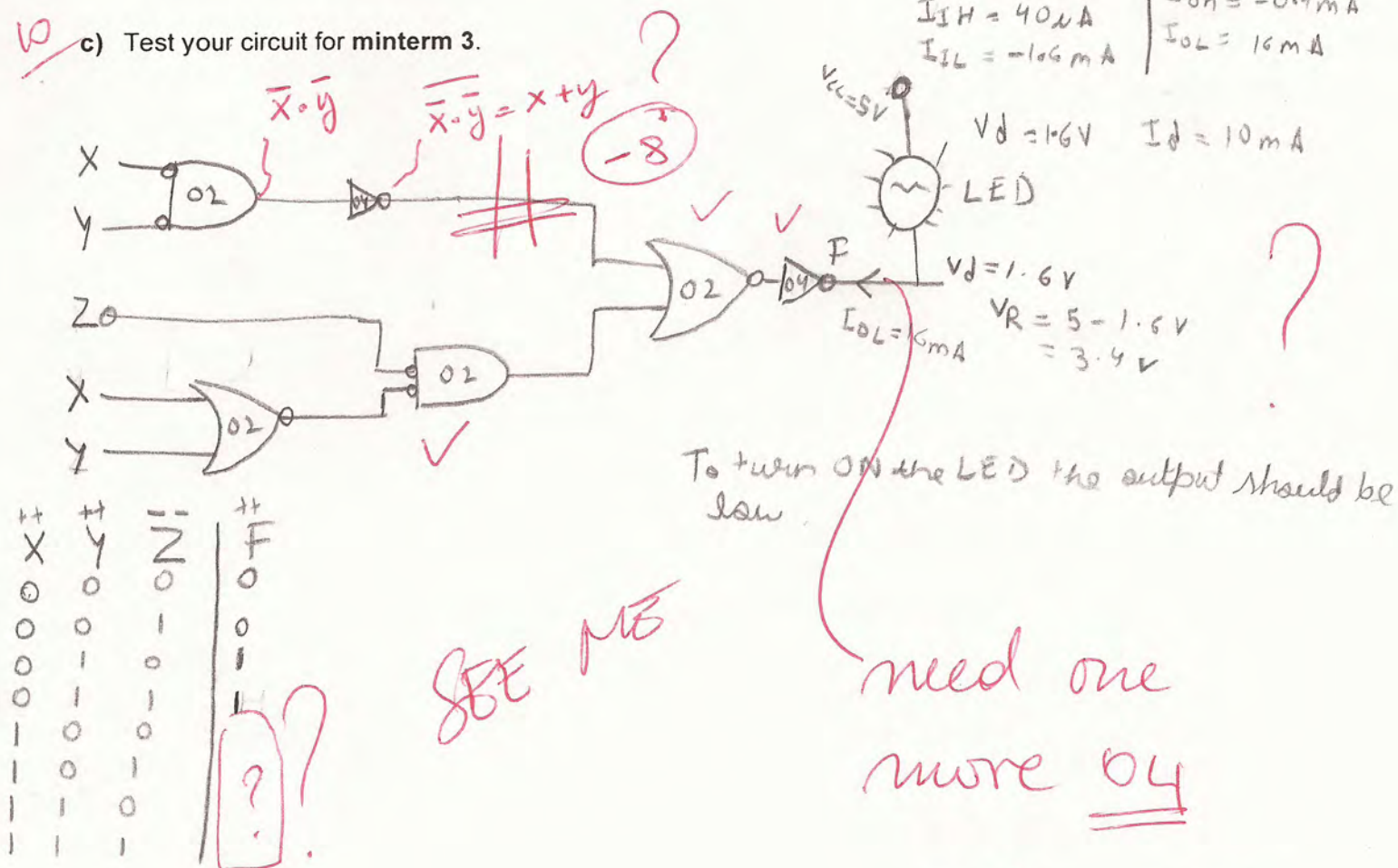

Test Circuit

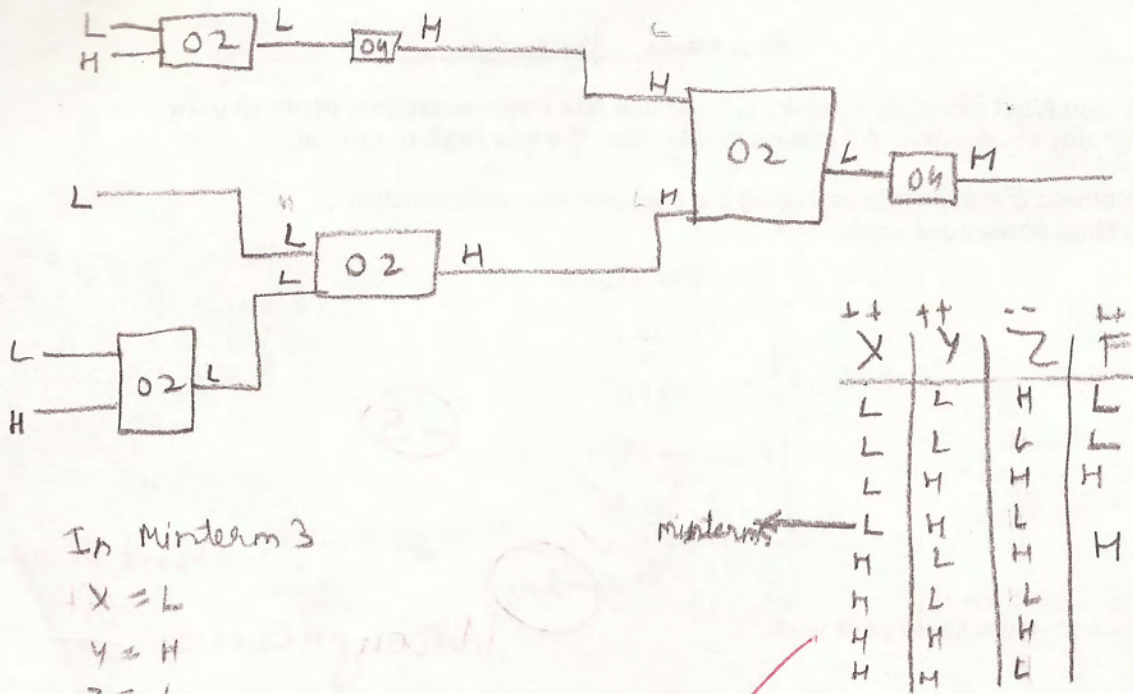

Hence, For Minterm 3 LED will not turn ON at output is High and $I_{OH} = 0.4 \text{ mA}$

how did you get this table?